

## ***AN-1304 LM5068 -48V Hot Swap Controller***

---

### **ABSTRACT**

This application report explains the function and design of components connected to MOSFET's gate terminal that limit inrush currents during insertion of a module into a live backplane when using the LM5068 without external current sense resistor.

---

### **Contents**

1	Introduction .....	2
2	Theory of Operation .....	2
3	Conclusion .....	4

### **List of Figures**

1	Typical Application Schematic.....	2
2	Calculation of Feedback Capacitor C2.....	3

## 1 Introduction


The LM5068 is a hot-swap controller that allows a circuit card to be safely inserted or removed from live backplane without having to shutdown the system power. The wide operating input voltage range (from  $-10\text{V}$  to  $-90\text{V}$ ) is well suited for  $-48\text{V}$  power systems. The LM5068 provides a current limited power to turn-on circuit cards thus preventing glitches on the power supply rail and damage to board connectors and components. The under-voltage and over-voltage protection of the LM5068 ensure that the input voltage is stable and within tolerance before applying power to the load.

## 2 Theory of Operation


The LM5068 is a hot-swap controller used as system supply monitor as well as current limiter. The system monitor function senses the supply voltage for under-voltage and over-voltage conditions and will shutdown the external MOSFET to stop power from flowing to load during these conditions. The current monitor functions to limit inrush current and output overload circuit current to prevent damage to the system.

The LM5068 has three current limit thresholds, at  $50\text{mV}$ ,  $100\text{mV}$  and  $200\text{mV}$ , to limit overload circuit current during output short-circuit or other overload conditions using a current sense resistor. From the above current limit thresholds, it is clear that overload current limit threshold of  $100\text{mV}$  (IACL, active current limit loop) is twice the circuit breaker (ICB) current limit of  $50\text{mV}$ , and the user doesn't always have the flexibility to set his inrush current limit to twice the steady state current limit threshold of  $50\text{mV}$ , due to application limitations. This application report describes an alternative approach to overcome these situations without the use of current-sense resistor.

In the application circuit shown in Figure 1, the input power to the module (shown here as load) is controlled by placing an N-channel external MOSFET switch in the power path. Resistors R1, R2 & R3 determine the UV and OV thresholds of the power supply input. Both the controller (LM5068) and the external MOSFET work together to limit the charging current when the board is first plugged into the live backplane. When the power is first applied to VDD, the controller holds the gate of the MOSFET (Q1) to ground. After a programmable debounce delay determined by the timer capacitor CT, an internal  $60\mu\text{A}$  current source begins to charge the MOSFET gate. The capacitor C2 and resistor R4 acts as a feedback network to accurately control the  $dv/dt$  and inrush current in the load capacitor CL. The drain voltage fall rate as the MOSFET turns on, is fed back to the gate terminal through R4 and C2, to appropriately control the gate voltage rise time. The MOSFET gate is supplied by a constant current source of  $60\mu\text{A}$ . The desired value of capacitor C2 can be calculated as follows. Refer to the schematic in Figure 2.

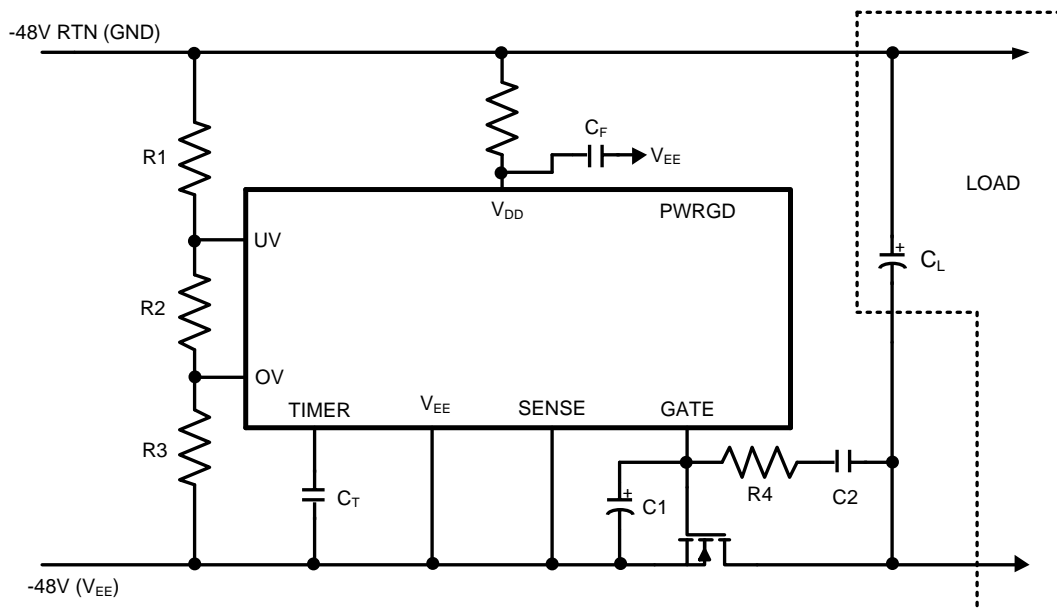

**Figure 1. Typical Application Schematic**

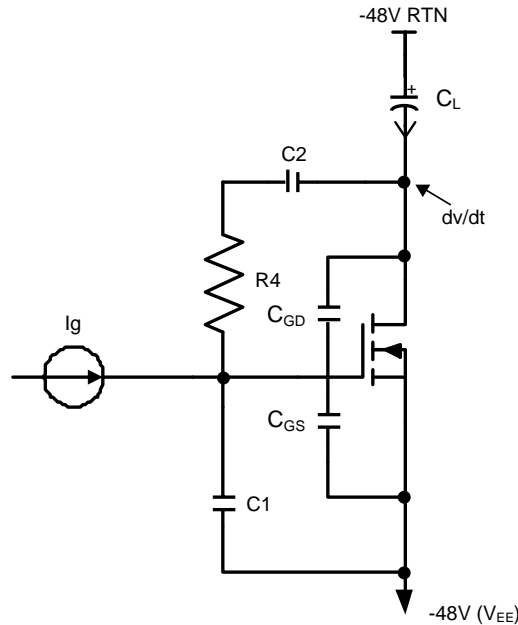

**Figure 2. Calculation of Feedback Capacitor C2**

The rate of change of drain voltage is given by,

$$\frac{dv}{dt} = \frac{I_g}{(C2 + C_{GD})} = \frac{I_{L(max)}}{C_L} \quad (1)$$

where  $I_g$  is the gate current source, and  $I_{L(max)}$  is the maximum inrush current that is allowed, and  $C_{GD}$  is the MOSFET's gate to drain capacitance.

From equation (1),  $C2$  can be calculated as

$$C2 + C_{GD} = C_L \times \frac{I_g}{I_{L(max)}} \quad (2)$$

$$C2 = C_L \times \frac{I_g}{I_{L(max)}} - C_{GD} \quad (3)$$

$R4$  is calculated to limit current and to have a maximum drop of less than a volt at  $60\mu A$  of MOSFET gate current, and to eliminate any kind of glitch at the gate terminal during normal operation or during plugging into the live backplane using  $R4$ ,  $C1$  filter. Capacitor  $C1$  and  $R4$  prevent  $Q1$  from turning on momentarily when the power pins first make contact. Without  $C1$  and  $R4$ , Capacitor  $C2$  would pull up the gate of  $Q1$  to approximately even before the LM5068 powers up and the pull-down of the gate is activated.

$$V_g = |V_{EE}| \times \frac{C2 + C_{GD}}{C_{GS}} \quad (4)$$

In the above equation,  $C_{GS}$  is the internal gate to source capacitance of the MOSFET. By placing capacitor  $C1$  in parallel with gate to source capacitance of  $Q1$ , this issue can be avoided. The value of  $C1$  is calculated as follows.

$$C1 \geq \left[ \frac{(V_{IN(max)} - V_{th})}{V_{th}} \times (C2 + C_{GD}) \right] - C_{GS} \quad (5)$$

where  $V_{th}$  is MOSFET's minimum gate threshold voltage and  $C_{GD}$  is the gate to drain capacitance of the MOSFET.

### 3 Conclusion

This application report describes the functionality of LM5068 hot-swap controller as a inrush current limiter and system monitor without using a current sense resistor. It should be understood that without sense resistor some features of LM5068 are disabled, including limiting output overload circuit current and excessive supply currents.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)