

**LM20125,LM26480,LM3743,LM3880,LMZ10504,
LMZ14203**

????FPGA????????????????????



Literature Number: ZHCA410

Power Supply Design Considerations for Modern FPGAs

— By Dennis Hudgins, Low Voltage Applications Manager, Tucson Design Center

Introduction

Today's FPGAs tend to operate at lower voltages and higher currents than their predecessors. Consequently, power supply requirements may be more demanding, requiring special attention to features deemed less important in past generations. Failure to consider the output voltage, sequencing, power-on, and soft-start requirements can result in unreliable power-up or potential damage to FPGAs.

Output Voltage Requirements

The first criteria to consider when designing power supplies for FPGAs are the voltage requirements for the different supply rails. Most FPGAs have specifications for the CORE and IO voltage rails and many require additional auxiliary rails that may power internal clocks, phase-lock loops or transceivers. *Table 1* provides the voltage levels and tolerances for some of the newest FPGAs.

Table 1. Voltage Requirements for Common Modern FPGAs

FPGA	Core	Core Tolerance	Auxiliary Power	Auxiliary Tolerance	IO Voltage*	IO Tolerance*
Spartan-6	1.2	5%	2.5 or 3.3	5%	1.2 to 3.3	1.1 to 3.45
Spartan-6 (-1L)	1.0	5%	2.5 or 3.3	5%	1.2 to 3.3	1.1 to 3.45
Virtex-6	1.0	5%	2.5	5%	1.2 to 2.5	1.14 to 2.625
Virtex-6 (-1L)	0.9	30 mV	2.5	5%	1.2 to 2.5	1.14 to 2.625
Stratix-IV (GX and E)	0.9	30 mV	2.5 (VCCA_PLL)	5%	1.2 to 3.0	5%
			0.90 (VCCD_PLL)	30 mV		
Stratix-IV (GT)	0.95	30 mV	2.5 (VCCA_PLL)	5%	1.2 to 3.0	5%
			0.95 (VCCD_PLL)	30 mV		
Cyclone-IV (GX)	1.2	40 mV	2.5	5%	1.2 to 3.3	5%
Cyclone-IV (E)	1.0	*	2.5	5%	1.2 to 3.3	5%
Arria-II	0.9	30 mV	2.5 (VCCA_PLL)	5%	1.2 to 3.3	5%
			0.90 (VCCD_PLL)	30 mV		

* Some values may differ slightly from those listed. Please consult your FPGA's associated documentation for details.

Power Supply Design Considerations for Modern FPGAs

Since FPGAs generally specify several permissible voltage levels for the IO, the voltage selected is dictated by the external digital circuitry. To provide flexibility, FPGAs will generally provide multiple IO banks that can be powered separately, allowing FPGAs to interface with various logic families. For simplicity, the solutions illustrated in this article will assume all IO banks are powered off of a single power supply rail. The core voltage supplies the internal logic configuration blocks of FPGAs and is where many of the internal digital path processes occur. As such, the current demanded by the core will vary greatly depending on the percent utilization of FPGAs. Vendors of the FPGAs described herein provide design tools that estimate core current requirements based on the internal blocks utilized.

Over time, the voltages used to power the core have steadily dropped. Modern cores utilize 65 nm, 45 nm or even 40 nm geometry silicon processes and may operate from voltages as low as 0.9V. These lower voltages are valuable to reduce power dissipation in FPGAs. The trade off, however, is that keeping within the voltage tolerance requirements becomes more challenging for the power supply designer.

Output Capacitance and Transient Considerations

A good power supply design will keep the core voltage within tolerance at all times. Most of the power supply transient concerns can be managed by properly selecting the bypass and bulk capacitances for the power supply. In general, every core ball or pin connection should be bypassed directly under FPGAs with high-quality X5R or X7R ceramic capacitors. The values recommended for each of these capacitors range from 1 μF to 10 μF and will generally be specified by FPGA manufacturers. These capacitors provide a charge when FPGAs need to rapidly draw large spikes of current during high speed operations. Likewise, the bulk capacitance should be selected to provide charge during large steps of current, which tend to occur during power-on, application-start, or a change in application state. Before increasing the amount of output capacitance to solve transient droop issues, changes to the power supply should be made that do not involve an increase in PCB area or component count.

The response to a load transient is dictated by the large signal response time that consists of ramping the inductor current to the correct operating level and the small signal response of the control loop.

Transient Response Optimizations

To optimize the transient response, ensure the supply is switching at the highest possible frequency. This will allow use of a small inductor and reduce the large signal response time. Typical high performance power supply solutions can be designed to have crossover frequencies as high as one-tenth to one-fifth the switching frequency. Pushing the crossover frequency too high may result in ringing at the output during a load transient indicating poor phase margin. Any ringing in the output should be avoided as this may result in instability with external component variation or when operating at temperature extremes.

AUX Voltage Considerations

Many FPGAs require a third power supply commonly referred to as the auxiliary rail or AUX. Since the AUX rail may power internal clocks, phase-lock loops, or transceivers, the amount of output voltage ripple on this rail should be minimized. In some cases, additional ferrite beads and capacitors filtering may be needed to meet the application or FPGA noise requirements. In applications where noise is extremely important, a low noise, high PSRR LDO, like the LP3878, should be considered instead of a switching converter.

Sequencing Requirements

The sequencing requirements vary depending on the particular FPGA being used and many newer FPGAs specify that no sequencing is required. While this is technically true for the FPGA, it is not the optimal way to design a power solution. National Semiconductor offers several devices to address sequencing requirements. The LM3880 is designed to address sequential sequencing of multiple supply rails. This device is available in a small SOT-23 package and can sequence up to three supply rails. Many options are available to control the up and down, three-flag outputs sequencing timing. National also provides devices to support customized flag order and timing.

Figure 1 illustrates a typical application circuit for the LM3880.

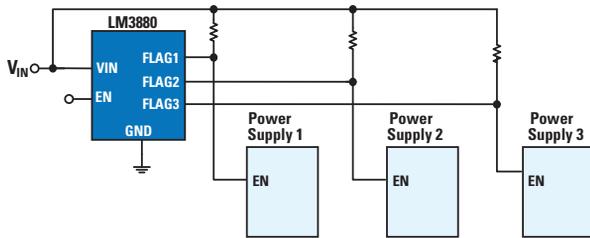


Figure 1. Simplified Buck Converter Schematic

Voltage tracking is another method of sequencing power supplies applicable to FPGAs and many processors. The most common and generally recommended method to power up FPGAs and other processors is to have the CORE voltage track the I/O voltage during startup as shown in Figure 2.

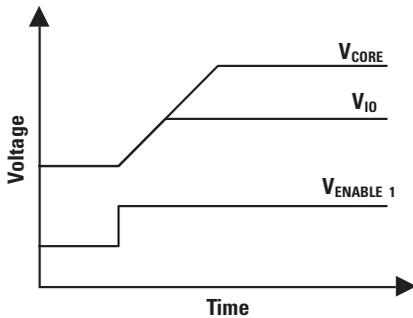


Figure 2. Startup voltage tracking

This power-up technique is known as simultaneous startup, and its primary advantage is that it avoids turning on any parasitic conduction paths that may exist between the CORE and IO supply rails. Turning on a parasitic conduction path may lead to unreliable startup or even damage to FPGAs or DSPs. Some of National's devices that feature voltage tracking include the LMZ14203 and LMZ10504 SIMPLE SWITCHER® Power Modules, the LM20k family of high performance synchronous DC/DC converters, as well as the LM3743 controller.

Figure 3 illustrates a typical voltage tracking configuration for these devices.

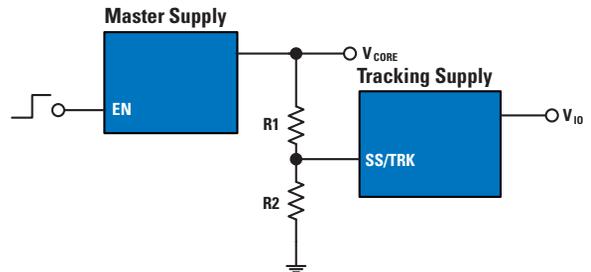


Figure 3. Typical voltage tracking configuration

Startup / Power-on Requirements

When sequential sequencing is used in systems with multiple voltage rails, as is the case with many FPGA solutions, it is likely that an output of one of the power supplies could be pre-biased through various parasitic conduction paths. In this situation, how the power supply handles this pre-biased state can have an impact on long term system reliability, or even the ability of the power supply or FPGAs to start successfully. To avoid the pitfalls associated with a pre-biased startup, the power supply should not pull the output low if a pre-biased condition exists. Figure 4 illustrates how a pre-biased condition should be handled when the output is pre-biased to three different voltage levels. All power solutions featured in this publication are capable of properly handling a pre-biased start up. Power supplies used to power both the CORE and IO must be monotonic during power-on to avoid FPGA startup problems. A monotonic startup continuously increases until the output reaches the final value.

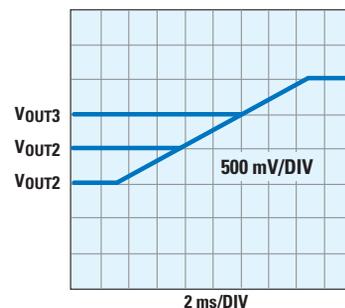


Figure 4. Pre-biased startup of the LM3743

Power Supply Design Considerations for Modern FPGAs

The critical area for monotonicity for most modern core voltage rails occurs between 0.5V to 0.9V. This is when FPGAs initialize the internal logic blocks to valid operating states.

Soft-start Requirements

Using soft-start is highly recommended, even if not specified by the FPGA manufacturer. Slowly ramping the input voltage reduces the inrush currents seen in some FPGAs. Using soft-start also reduces the current needed to charge the output capacitance of the power supply and will decrease the voltage droop on the input bus during startup.

The startup or soft-start requirements for several FPGAs are summarized in *Table 2*.

Table 2. Required Startup/Soft-start Times

FPGA	Min	Max
Spartan-6 (-3 & -2 Speeds)	0.20 ms	50 ms
Spartan-6 (-1L speed grade)	0.20 ms	40 ms
Virtex-6	0.20 ms	50 ms
Cyclone IV (Normal POR)	0.050 ms	50 ms
Cyclone IV (Fast POR)	0.050 ms	3 ms
Stratix-IV (Normal POR)	0.050 ms	100 ms
Stratix-IV (Fast POR)	0.050 ms	4 ms
Arria-II GX (Normal POR)	0.050 ms	100 ms
Arria-II GX (Fast POR)	0.050 ms	4 ms

A startup time of 10 ms generally limits the capacitive inrush currents to an acceptable level while meeting the requirements for most FPGAs and DSPs.

Application Examples

The application examples shown to the right implement requirements previously discussed for powering FPGAs. These solutions are meant to be guidelines for selecting the correct devices and circuit topologies to meet FPGA power requirements.

Figure 5 uses the synchronous LMZ14203 SIMPLE SWITCHER Power Module, capable of supplying 3A of output current. This newly-released device not only includes the power switches, but also the inductor inside the package. This reduces the component design and procurement process to just a few capacitors and resistors. The inductor's inclusion in the package also simplifies layout complexities because of the reduced loop area with large di/dT transitions. This, coupled with the inductor's shielded design, reduces EMI and National Semiconductor tested its evaluation boards to comply with the EN55022 Class B specification.

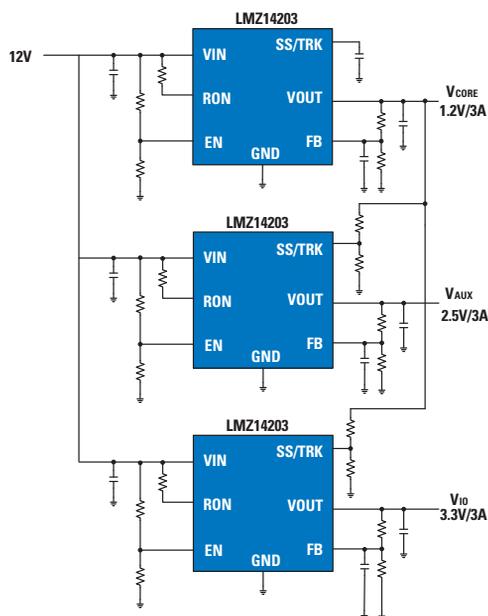


Figure 5. 3A Core and I/O Solution from 12V Bus

As an added benefit, the SIMPLE SWITCHER power module families use a 7 lead TO-263-like package and each family is pin-to-pin compatible, providing an easy path to support different current levels. The packaging lends itself very well to hand-soldered prototypes while the exposed pad on the bottom conducts heat out of the package and enables a very low θ_{JA} of 20°C per watt.

This solution is ideal for lower output current FPGAs and features a monotonic startup with voltage tracking.

The LMZ14203 includes many fault protection features such as over-voltage protection (OVP), under-voltage protection (UVP), thermal shutdown, and an accurate current limit. The synchronous operation of the LMZ14203 offers improved efficiency over non-synchronous devices resulting in cooler operation and increased reliability.

Figure 6 illustrates the LMZ10504 SIMPLE SWITCHER Power Module being used to power an FPGA for load currents up to 4A. Similar to the LMZ14203, this newly-released device includes the power switches and inductor inside the package, thus sharing the same easy design-in process. This full-featured device operates at a fixed 1 MHz switching frequency and offers voltage tracking, programmable soft-start, and 1.5% voltage accuracy at the feedback pin. The LMZ10504 achieves efficiencies as high as 96% and features the same protection features as the LMZ14203 while also sharing its 7 lead TO-263-like package. Both devices are fully supported by WEBENCH® Power Designer.

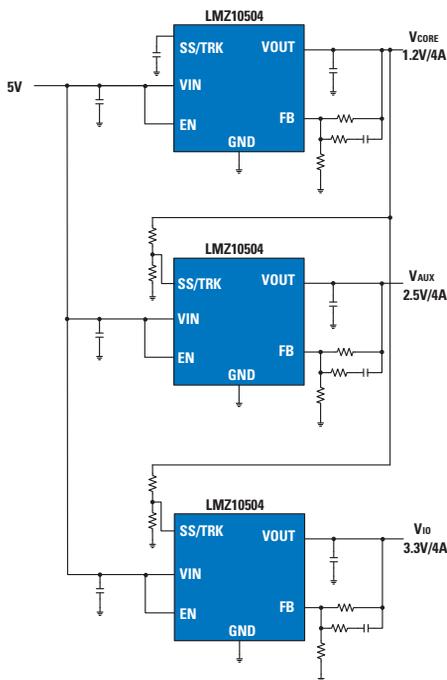


Figure 6. 4A Core and I/O Solution from 5V Bus

Figure 7 features the LM26480 PMIC to provide the CORE, IO and AUX voltages from a single device. This device integrates dual switching regulators with a current capability of up to 1.5A each and dual LDOs with a current capability of up to 300 mA each. This high degree of integration makes the LM26480 an ideal solution for use with the Cyclone and Spartan families of FPGAs. This solution provides a monotonic startup with internal soft-start to limit inrush startup currents. Sequencing is performed with the LM3880. The startup sequence will be the CORE followed by the IO, and then by the AUX rails. The LM3880 features an integrated precision enable circuit that allows the user to set the turn on voltage with two external resistors.

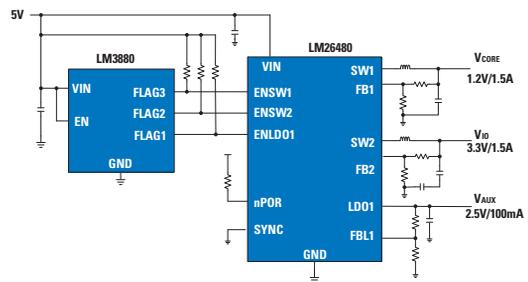


Figure 7. Externally-Sequenced Single Chip FPGA Power Supply

The circuit shown in *Figure 8* utilizes the LM3743 for powering both the CORE and IO. This controller is capable of supporting designs up to 20A and features a SS/TRACK pin to provide a monotonic simultaneous startup. The LM3743 provides increased system reliability by offering both high- and low-side current limit as well as output under-voltage protection. The device also features a hiccup mode protection that eliminates thermal runaway during fault conditions.

The LM20125 is used to power the auxiliary voltage rail and has a compatible SS/TRK pin. This synchronous buck regulator utilizes emulated current mode control and uses nonlinear slope compensation to ease design-in. The LM20125 is a 5A-capable device with efficiencies as high as 97% due to the 35 mΩ integrated FETs.

Power Supply Design Considerations for Modern FPGAs

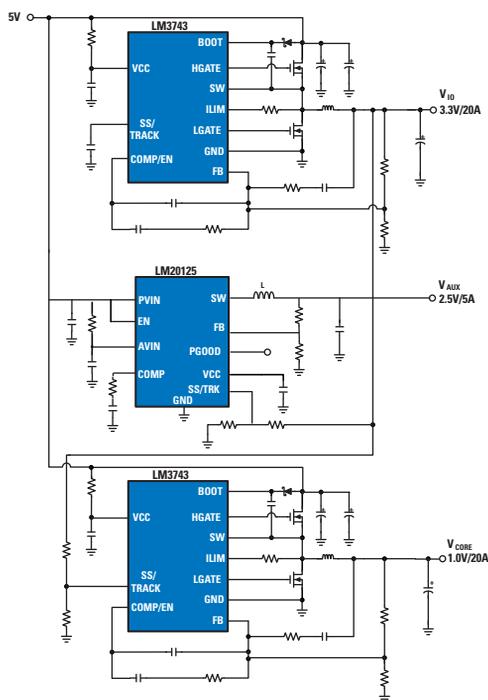


Figure 8. High current LM3743-based power supply solution.

The LM201xx family of devices shares the same pin-out so higher or lower currents can be obtained by interchanging devices. The LM20125 is offered in a small TSSOP-16 package and is fully supported by WEBENCH Power Designer.

National offers a wide range of products that support the power requirements of the latest generation of FPGAs. These power solutions can support the sequencing, soft-start, and voltage tolerance requirements for the newest families of FPGAs, as well as handle challenges such as pre-biased outputs and demanding transient response needs. For your complete FPGA power supply needs, please visit www.national.com. ■

References

1. *LMZ14203 Product Datasheet* - <http://www.national.com/ds/LM/LMZ14203.pdf>
2. *LMZ10504 Product Datasheet* - <http://www.national.com/ds/LM/LMZ10504.pdf>
3. *LM3880 Product Datasheet* - <http://www.national.com/ds/LM/LM3880.pdf>
4. *LM26480 Product Datasheet* - <http://www.national.com/ds/LM/LM26480.pdf>
5. *LM20125 Product Datasheet* - <http://www.national.com/ds/LM/LM20125.pdf>
6. *LM3743 Product Datasheet* - <http://www.national.com/ds/LM/LM3743.pdf>
7. *Cyclone IV Device Handbook* - <http://www.altera.com/literature/hb/cyclone-iv/cyclone4-handbook.pdf>
8. *Arria II Device Handbook* - http://www.altera.com/literature/hb/arria-ii-gx/arria-ii-gx_handbook.pdf
9. *Stratix IV Device Handbook* - http://www.altera.com/literature/hb/stratix-iv/stratix4_handbook.pdf
10. *Virtex-6 Product Information* - <http://www.xilinx.com/products/virtex6/>
11. *Spartan-6 Product Information* - <http://www.xilinx.com/products/spartan6/index.htm>

Power Design Tools



Design, build, and test analog circuits in this online design and prototyping environment.
national.com/webench



Expand your knowledge and understanding of analog with our free online educational training tool.
national.com/training



National's monthly analog design technical journal.
national.com/edge

Tools for Energy-Efficient Designs

Access white papers, reference designs, and application notes on PowerWise® products and systems.

www.national.com/powerwise

National Semiconductor
2900 Semiconductor Drive
Santa Clara, CA 95051
1 800 272 9959

Mailing address:
PO Box 58090
Santa Clara, CA 95052

Visit our website at:
www.national.com

**For more information,
send email to:**
support@nsc.com

Don't miss a single issue!

Subscribe now to receive email alerts when new issues of Power Designer are available:

national.com/powerdesigner

Read our Signal Path Designer® online today at:

national.com/spdesigner



重要声明

德州仪器(TI) 及其下属子公司有权在不事先通知的情况下, 随时对所提供的产品和服务进行更正、修改、增强、改进或其它更改, 并有权随时中止提供任何产品和服务。客户在下订单前应获取最新的相关信息, 并验证这些信息是否完整且是最新的。所有产品的销售都遵循在订单确认时所提供的TI 销售条款与条件。

TI 保证其所销售的硬件产品的性能符合TI 标准保修的适用规范。仅在TI 保证的范围内, 且TI 认为有必要时才会使用测试或其它质量控制技术。除非政府做出了硬性规定, 否则没有必要对每种产品的所有参数进行测试。

TI 对应用帮助或客户产品设计不承担任何义务。客户应对其使用TI 组件的产品和应用自行负责。为尽量减小与客户产品和应用相关的风险, 客户应提供充分的设计与操作安全措施。

TI 不对任何TI 专利权、版权、屏蔽作品权或其它与使用了TI 产品或服务的组合设备、机器、流程相关的TI 知识产权中授予的直接或隐含权限作出任何保证或解释。TI 所发布的与第三方产品或服务有关的信息, 不能构成从TI 获得使用这些产品或服务的许可、授权、或认可。使用此类信息可能需要获得第三方的专利权或其它知识产权方面的许可, 或是TI 的专利权或其它知识产权方面的许可。

对于TI 的产品手册或数据表, 仅在没有对内容进行任何篡改且带有相关授权、条件、限制和声明的情况下才允许进行复制。在复制信息的过程中对内容的篡改属于非法的、欺诈性商业行为。TI 对此类篡改过的文件不承担任何责任。

在转售TI 产品或服务时, 如果存在对产品或服务参数的虚假陈述, 则会失去相关TI 产品或服务的明示或暗示授权, 且这是非法的、欺诈性商业行为。TI 对此类虚假陈述不承担任何责任。

TI 产品未获得用于关键的安全应用中的授权, 例如生命支持应用(在该类应用中一旦TI 产品故障将预计造成重大的人员伤亡), 除非各方官员已经达成了专门管控此类使用的协议。购买者的购买行为即表示, 他们具备有关其应用安全以及规章衍生所需的所有专业技术和知识, 并且认可和同意, 尽管任何应用相关信息或支持仍可能由TI 提供, 但他们将独力负责满足在关键安全应用中使用其产品及TI 产品所需的所有法律、法规和安全相关要求。此外, 购买者必须全额赔偿因在此类关键安全应用中使用TI 产品而对TI 及其代表造成的损失。

TI 产品并非设计或专门用于军事/航空应用, 以及环境方面的产品, 除非TI 特别注明该产品属于“军用”或“增强型塑料”产品。只有TI 指定的军用产品才满足军用规格。购买者认可并同意, 对TI 未指定军用的产品进行军事方面的应用, 风险由购买者单独承担, 并且独力负责在此类相关使用中满足所有法律和法规要求。

TI 产品并非设计或专门用于汽车应用以及环境方面的产品, 除非TI 特别注明该产品符合ISO/TS 16949 要求。购买者认可并同意, 如果他们在汽车应用中使用任何未被指定的产品, TI 对未能满足应用所需要求不承担任何责任。

可访问以下URL 地址以获取有关其它TI 产品和应用解决方案的信息:

	产品		应用
数字音频	www.ti.com.cn/audio	通信与电信	www.ti.com.cn/telecom
放大器和线性器件	www.ti.com.cn/amplifiers	计算机及周边	www.ti.com.cn/computer
数据转换器	www.ti.com.cn/dataconverters	消费电子	www.ti.com/consumer-apps
DLP® 产品	www.dlp.com	能源	www.ti.com/energy
DSP - 数字信号处理器	www.ti.com.cn/dsp	工业应用	www.ti.com.cn/industrial
时钟和计时器	www.ti.com.cn/clockandtimers	医疗电子	www.ti.com.cn/medical
接口	www.ti.com.cn/interface	安防应用	www.ti.com.cn/security
逻辑	www.ti.com.cn/logic	汽车电子	www.ti.com.cn/automotive
电源管理	www.ti.com.cn/power	视频和影像	www.ti.com.cn/video
微控制器 (MCU)	www.ti.com.cn/microcontrollers		
RFID 系统	www.ti.com.cn/rfidsys		
OMAP 机动性处理器	www.ti.com/omap		
无线连通性	www.ti.com.cn/wirelessconnectivity		
	德州仪器在线技术支持社区		www.deyisupport.com

邮寄地址: 上海市浦东新区世纪大道 1568 号, 中建大厦 32 楼 邮政编码: 200122
Copyright © 2011 德州仪器 半导体技术 (上海) 有限公司