

Isolated RS-485 Reference Design

Thomas Kugelstadt

ICP - Industrial Interface

This design note presents the reference designs of isolated RS-485 nodes, using bus voltages of 3.3 V and 5 V. Various transceivers are used to satisfy the requirements for low, medium, and high data rates, as well as to accommodate the need for half- and full-duplex operation. [Table 1](#) lists the family of isolated RS-485 transceivers from Texas Instruments.

Table 1. Isolated RS-485 Transceivers

Device	Transmission	Data Rate [Mbps]	Rise Time [ns] (Typical)	Primary-Supply Voltage Range [V]	Secondary-Supply Voltage Range [V]
ISO3082	Half-duplex	0.2	900	3.15 – 5.5	4.5 – 5.5
ISO15		1	185	3.15 – 3.6	3.15 – 3.6
ISO3088		20	7	3.15 – 5.5	4.5 – 5.5
ISO3080	Full-duplex	0.2	900	3.15 – 5.5	4.5 – 5.5
ISO35		1	185	3.15 – 3.6	3.15 – 3.6
ISO3086		20	7	3.15 – 5.5	4.5 – 5.5

Signal-Path Isolation

All transceivers present a 1/8 unit load to the bus, possess a 4-kV peak isolation voltage, and have a typical transient immunity of 50 kV/μs. Whereas the ISO15 and ISO35 (shaded cells in Table 1) operate from a 3.3-V nominal supply on both the primary side and the secondary side, the transceivers of the ISO308x family allow for mixed-supply operation. This is of particular advantage for applications operating in harsh industrial environments, because the 3.3 V on the primary side enables the connection to low-voltage microcontrollers for power preservation, whereas the 5 V on the secondary side maintains a high signal-to-noise ratio when driving signals across long distances.

Power Supply Isolation

Modern isolated power supplies are available as small, surface-mount modules. They often include the transformer driver, the actual isolation transformer, and the rectifier network. Sophisticated DC-DC modules, such as the RSZ-3.33.3HP (3.3 Vin/3.3 Vout) and RSZ-3.305HP (3.3 Vin/5 Vout), even include a linear regulator with its associated bypass and output capacitors, while providing short-circuit protection and a solid, 2-kV isolation voltage.

Noise and Transient Suppression

For effective transient protection, a low-capacitive transient voltage suppressor (TVS), such as PSM712, is recommended. The device provides a 600-W surge capability, 75 pF of capacitance, and up to 40-kV ESD protection, while its stand-off voltages cover the RS-485 common-mode range of –7 V to +12 V.

Implementation of additional noise filtering to the signal paths between the node controller and the single-ended side of the transceiver through simple R-C low-pass filters is recommended. Calculate the filter component values such that $R_F \times C_F = 0.032 / f_s$ with f_s being the highest signal frequency of interest.

System Diagrams

Figure 1 shows the system diagram for a 3.3-V/5-V, half-duplex network node using ISO3082 for signal isolation and RSZ-3.305HP for power isolation. Figure 2 shows the system diagram for a 3.3-V/3.3-V, full-duplex network node using ISO35 for signal isolation and RSZ-3.33.3HP for power isolation.

References

For more specific information on devices presented in this design note, see one of the following links:

- For isolated RS-485 transceivers see www.ti.com
- For isolated DC-to-DC modules see www.recom-power.com or www.recom-international.com
- For transient voltage suppressors see www.protekdevices.com

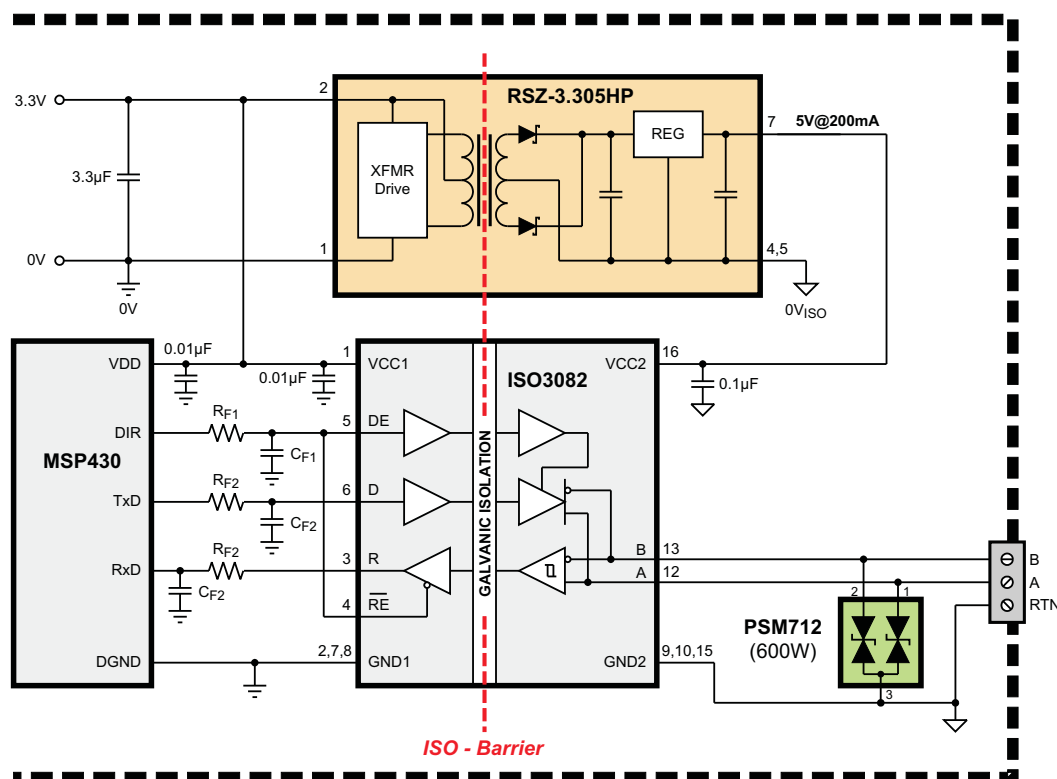


Figure 1. 2-kV, Isolated RS-485 Node for 200-kbps, Half-Duplex Operation

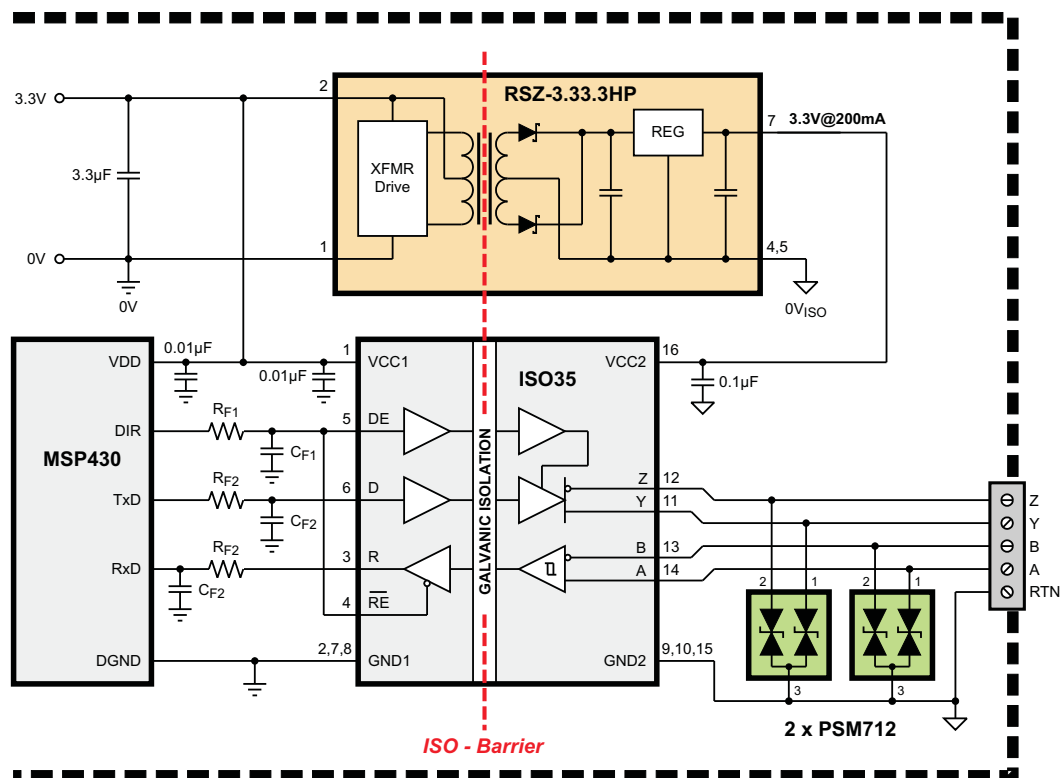


Figure 2. 2-kV, Isolated RS-485 node for 1-Mbps, Full-Duplex Operation

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2009, Texas Instruments Incorporated