

Speed-Control Techniques in AC-DC Operated BLDC Applications

Naveen Bevara
Sanjay Dixit

BLDC Motor Drivers

ABSTRACT

To achieve energy efficiency, ceiling fans and ventilation fans are moving from simple alternate-current (AC) induction motors to brushless direct-current (DC) motors (BLDC). An AC-operated BLDC motor requires two sections to run the BLDC motor: the AC-DC power conversion section and the DC to 3-phase AC conversion section. The Texas Instruments reference design, [TIDA-00652](#), helps to meet these challenges of higher efficiency and power factor in a simpler way by using a single-stage power supply to convert the AC mains input into a low-voltage DC output. This reference design also combines a fully integrated and well protected single-chip, DRV10983, sensor-less sinusoidal brushless motor controller for low-noise operation.

For the DRV10983 device, the motor can be controlled directly through PWM, analog, or I²C inputs. With the physical arrangement of ceiling fans, the speed control of an AC-operated BLDC motor can be possible with an infrared (IR) remote or any high-end wireless control. The speed can also be varied with a change in the supply voltage of the DRV10983 device, but with the variation of AC over universal range, the output of AC-DC is regulated to 24 VDC. Therefore the speed of the fan is controlled by providing a fixed DC or PWM signal at the SPEED pin of the DRV10983 device. The speed of the fan can also be controlled using the I²C input of the DRV10983 device, as demonstrated in the TIDA-00652 reference design.

This application report presents two different ways to control the AC-operated BLDC ceiling fan with existing infrastructure. The first solution is to vary the speed by only toggling the AC mains switch. The second solution is to vary the speed using the TRIAC component similar to an existing AC-operated ceiling fan.

Contents

1	Speed Control of BLDC motor by toggling the AC mains switch	3
1.1	Introduction	3
1.2	Additional Circuit Using CD74HC4017 and SN74HCT14	4
2	TRIAC Control of BLDC Motor	6
2.1	Optocoupler Circuit to Detect the Firing Angle.....	6
2.2	Additions to Input Filter for TRIAC Operation	8
3	References	9

List of Figures

1	BLDC Ceiling Fan Demonstrated in TIDA-00652.....	3
2	Modified Block Diagram.....	3
3	Proposed Solution to Control the Speed of the Fan by Toggling AC	5
4	Probable LED Arrangement to Indicate the Speed of Fan	6
5	TRIAC-Based Control of AC Operated BLDC Fan	7
6	PWM Signal at Emitter of Optocoupler	7
7	TRIAC Current and Input Rectified Voltage Without RC-Damped Circuit.....	8
8	TRIAC Current and Input Rectified Voltage With RC-Damped Circuit	8

All trademarks are the property of their respective owners.

9	Input Resistor and RC-Damping Circuit Added to Input Filter	8
---	-------------------------------------------------------------------	---

1 Speed Control of BLDC motor by toggling the AC mains switch

1.1 Introduction

Figure 1 shows a basic block diagram for an AC-operated BLDC ceiling fan demonstrated using the TIDA-00652 reference design.

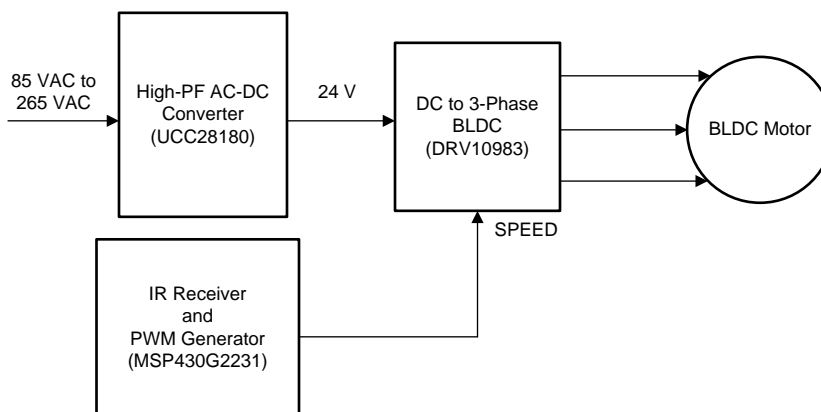


Figure 1. BLDC Ceiling Fan Demonstrated in TIDA-00652

With the addition of a proposed circuit to the existing solution, the speed can be controlled by only toggling the AC mains switch. The proposed solution can completely eliminate the option of a remote to reduce the cost of the microcontroller (MCU), remote, and IR receiver. These devices can be replaced by a low-cost solution based on a ring counter (TI's CD74HC4017 device) and inverter (TI's SN74HCT14 device) which varies the speed by only toggling the AC mains and avoids the cost of a TRIAC component which are used in conventional ceiling fans. This solution can also be used along with the IR remote solution and can be used as additional control in case of the remote is lost.

In addition, using the proposed solution, an arrangement of sequence LEDs can be implemented on the surface of the fan to indicate the speed of the fan. Figure 3 shows this modification of the proposed solution.

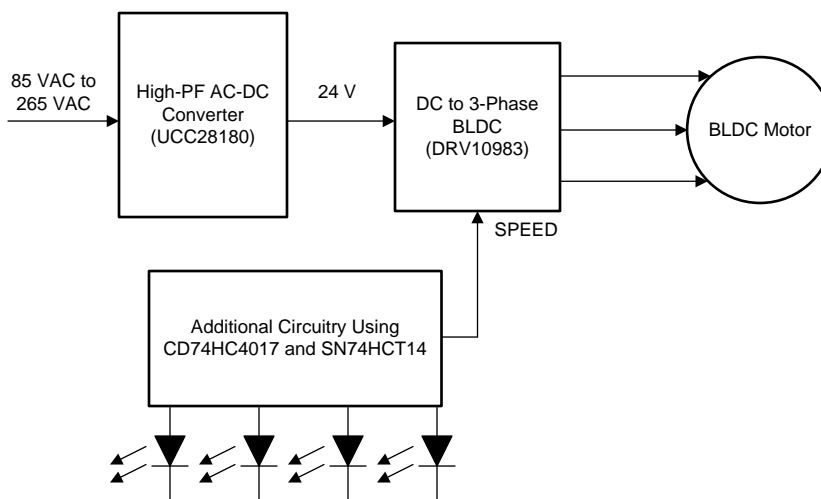


Figure 2. Modified Block Diagram

1.2 Additional Circuit Using CD74HC4017 and SN74HCT14

Figure 3 shows the working of an additional circuit. Whenever the AC is turned on, 24 V is formed at the output of the AC-DC section which is fed to the DRV10983 device. A 5-V supply is then formed to CD74HC4017 and 74HCT4017 using a Zener diode of 5V1. The 24 V is divided using a resistor divider and fed to the SN74HCT14 device to form 5 V at the input. If the AC is turned off, 24 V goes to zero making the input of Inverter to zero and, because the 5-V supply is still present because of a high capacitor value, the output of inverter is high. And now, if the AC is turned on again, 24 V is formed at the AC-DC section and gives a high signal at the input of the inverter. The high signal at the input of the inverter provides a high-to-low signal at the output which is fed to the clock of the counter resulting in a change of the output state. Therefore, with each toggle of the AC mains Q0, Q1, Q2, and Q3 turn on consecutively. With each signal output, the resistor divider network forms different voltages between 0 and 3.3 V in four different levels that can be fed to the SPEED pin of the DRV10983 device for different speeds of the fan. Q4 is connected to the master reset (MR) to revert back to initial step. The number of steps of speed can be increased by increasing the use of the number of outputs and adjusting the resistor divider network accordingly.

 


Figure 3. Proposed Solution to Control the Speed of the Fan by Toggling AC

To achieve four different steps of speed, 0.8 V, 1.6 V, 2.4 V, and 3.3 V must be generated at the output of the network. If 20 k Ω is used at the output, the R4, R5, R6, and R7 resistors must be used at the outputs of the ring counter.

$$\text{When Q0 is ON, } R4 = ((20 \text{ k}\Omega / 0.8) \times 5 \text{ V}) - 20\text{k} = 105 \text{ k}\Omega \quad (1)$$

$$\text{When Q1 is ON, } R5 = ((20 \text{ k}\Omega / 1.6) \times 5 \text{ V}) - 20\text{k} = 42.5 \text{ k}\Omega \quad (2)$$

$$\text{When Q2 is ON, } R6 = ((20 \text{ k}\Omega / 2.4) \times 5 \text{ V}) - 20\text{k} = 21.67 \text{ k}\Omega \quad (3)$$

$$\text{When Q3 is ON, } R7 = ((20 \text{ k}\Omega / 3.3) \times 5 \text{ V}) - 20\text{k} = 10 \text{ k}\Omega \quad (4)$$

In the schematic, the closest available resistor values were used

In addition, the output of Q0, Q1, Q2 and Q3 can be used to create an LED indication as shown in [Figure 4](#). Whenever Q0 turns on, one LED turns on, and when Q1 turns on, two LEDs turn on, and so on. These LEDs can be kept on the surface of the ceiling fan which appears as a circle and variation of speed can be indicated with variation in size of circle accordingly.


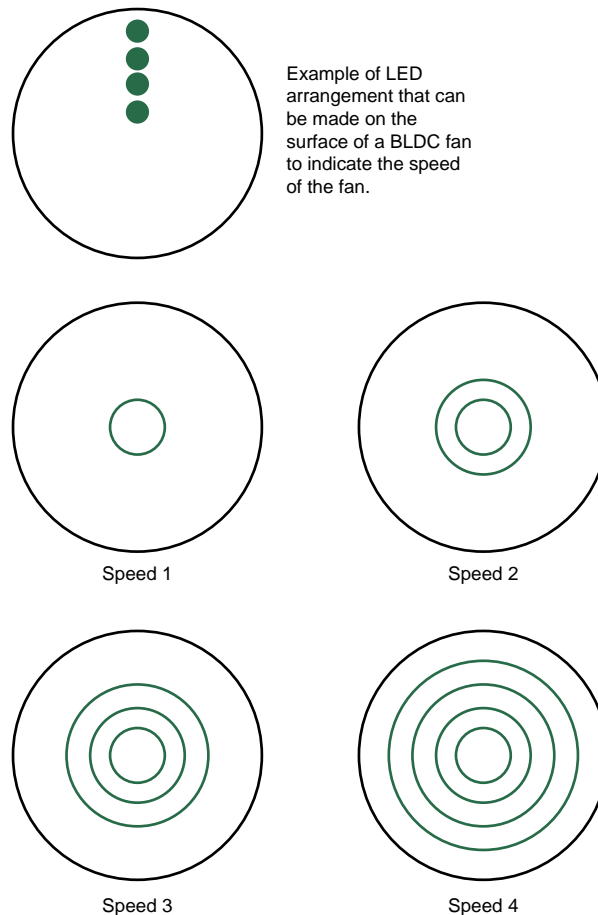


Figure 4. Probable LED Arrangement to Indicate the Speed of Fan

2 TRIAC Control of BLDC Motor

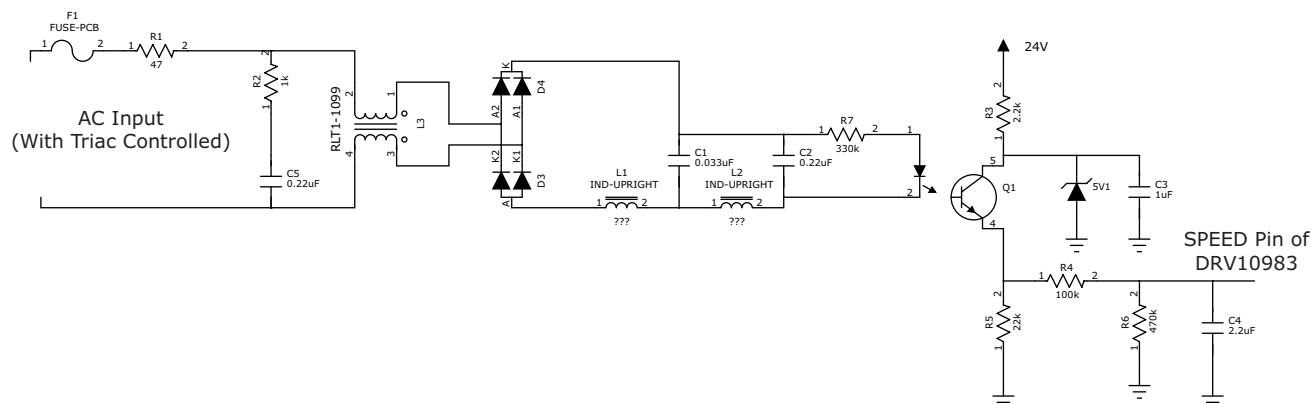2.1 Optocoupler Circuit to Detect the Firing Angle

In a BLDC motor, the variation of RMS AC source does not change the output DC. The TIDA-00652 reference design (BLDC ceiling fan TI Design) is used to implement TRIAC-based fan control. A small optocoupler-based circuit is connected to the TIDA-00652 BLDC board as shown in [Figure 5](#). The rectified AC is sensed using the optocoupler. As the phase angle of TRIAC is varied, a PWM signal is generated accordingly. The average of PWM is fed to the SPEED pin of the DRV10983 device.



Copyright © 2016, Texas Instruments Incorporated

Figure 5. TRIAC-Based Control of AC Operated BLDC Fan

The AC waveform chopped with a TRIAC at a certain firing angle generates a PWM signal corresponding to the firing angle as shown in Figure 6. This PWM signal is averaged using the RC low-pass filter. The variation in the PWM signal from 10% to 90% results in analog voltage from 0.8 V to 3.3 V correspondingly. The DRV10983 device can be used in Analog control mode and this output analog voltage can be connected to the SPEED pin of the DRV10983 device.

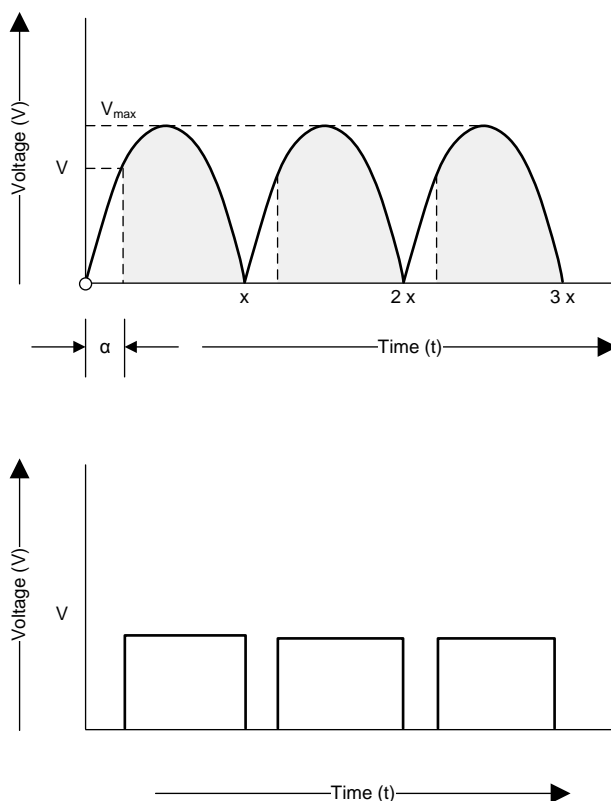


Figure 6. PWM Signal at Emitter of Optocoupler

2.2 Additions to Input Filter for TRIAC Operation

The resonance of the undamped EMI filter causes the input current, $i_{in}(t)$ to oscillate in response to the step change in the input voltage caused by the TRIAC firing action. Each time the input current falls below the holding current, I_{TH} , the TRIAC commutates off. The internal RC timer initiates a new firing sequence leading to repeated firing and misfiring of the TRIAC. Therefore the transient response of the EMI filter must be controlled by incorporating suitable damping circuits. The standard method is to use RC snubber as shown in Figure 9.

A small value selected for R_2 will cause the pole to move away from the zero while a large value for R_2 will lead to insufficient damping of complex filter poles. As a result, a small optimal range of resistance between $100\ \Omega$ and $2\ k\Omega$ exists, which leads to a non-zero input current. This value can either be iteratively derived using simulation software or empirically estimated based on experimental data.

The TRIAC-chopped AC looks similar to the waveform shown in Figure 7. With addition of an R and C snubber, false triggering is eliminated and should result in the waveform shown in Figure 8.

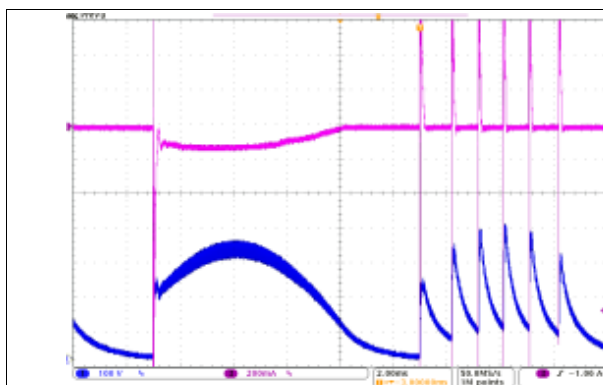


Figure 7. TRIAC Current and Input Rectified Voltage Without RC-Damped Circuit


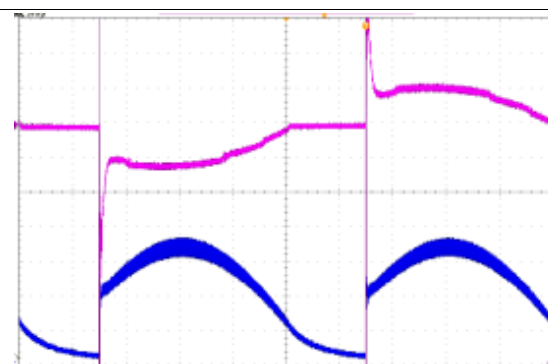


Figure 8. TRIAC Current and Input Rectified Voltage With RC-Damped Circuit

Rapid charging of the EMI filter capacitance during the firing sequence causes a large inrush current to flow through the TRIAC. A single series resistor, R_1 , shown in Figure 9, is required to limit the inrush current. The resistor also damps any high frequency oscillations caused by the internal TRIAC inductance or parasitic inductance and the EMI filter capacitance. The value of R_1 is generally in the range of $10\ \Omega$ to $100\ \Omega$ and is limited by the acceptable power loss and efficiency. Improvement in efficiency is achieved by incorporating an active MOSFET-based bypass circuitry at the cost of additional components.

Figure 9 shows the addition of the R_i and RC snubber in the input filter section with the previously mentioned considerations.

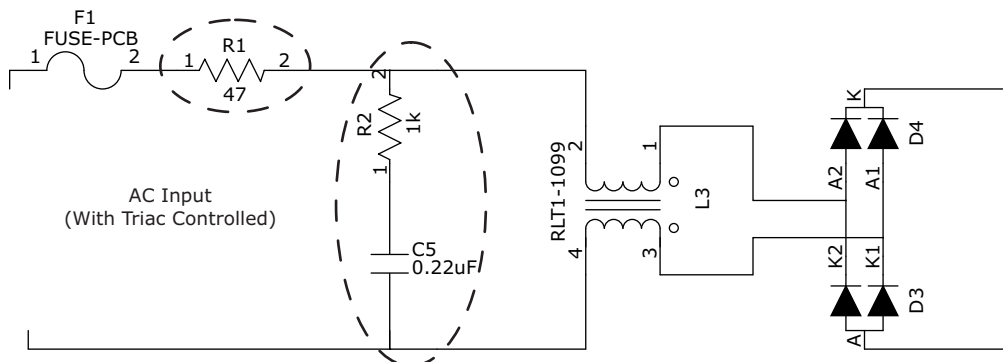

Copyright © 2016, Texas Instruments Incorporated

Figure 9. Input Resistor and RC-Damping Circuit Added to Input Filter

3 References

- [90- to 265-V AC, 91% Efficiency, >0.94 PF Buck-PFC Plus 24-V, 30-W Brushless DC Motor Drive Reference Design](#) (TIDUAS3)
- CD74HC4017 [High Speed CMOS Logic Decade Counter/Divider with 10 Decoded Outputs](#) (SCHS200)
- [DRV10983 12- to 24-V, Three-Phase, Sensorless BLDC Motor Driver](#) (SLVSCP6)
- M.D. Singh, K.B. Khanchandani, Power Electronics, Second Edition, Tata McGraw-Hill Education, 2007.
- Montu Doshi, James Patterson ; Lighting Power Products, Texas Instruments, Inc., Longmont, Colorado; "Input filter design for TRIAC dimmable LED lamps," IEEE Energy Conversion Congress and Exposition, Sept. 2013, pp. 4631 – 4638.
- SN74HCT14 [Hex schmitt-trigger inverters](#) (SCLS225)

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com