

Bi-Directional, Low-Side Phase Current Sensing with Integrated Over-Current Detection

Arjun Prakash, Current Sensing Products



Sensors are critical in a motor control application. Sensors provide valuable information such as torque, temperature, position and speed. Today's advancements in sensor technologies have enabled improvements in accuracy, performance, cost and reliability. Today's technology also allows for integration of multiple features within a sensor that are focused on solving system level challenges. In motor control, several sensors are being used for feedback and protection. One of the key components for motor control feedback and protection is the current sense amplifier.

Low-side Phase Current Sensing

In a motor control for DC brushed or brushless drive architectures, low-side current sensing is one of the most cost effective solutions to measure currents due to lower common mode. Low-side sensing is accomplished using an external shunt connected between the controller ground and the system ground as shown in Figure 1. One of the fundamental requirements for using low-side sensing is that the amplifier should be able to support common mode voltages below ground. As the external shunt is connected between the controller ground and system ground, it is critical that the layout of the shunt and current sense amplifier be optimized to maximize current measurement accuracy. Current sense amplifiers from Texas Instruments are specifically designed and factory trimmed to ensure the overall system errors.

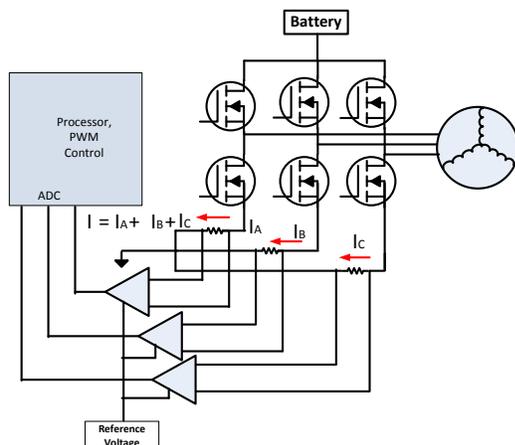


Figure 1. Low-Side Current Sensing

Bi-Directional Low-Side Phase Current Sensing

In a motor control application, especially for higher power systems, it is critical that the motor is very well protected against excessive currents. When excessive currents are passed through the motor due to overheating, the coil within the motor can cause failures leading to a permanent motor damage.

Figure 2 illustrates that when the controller switches from phase1 to phase2, for a brief period of time the motor acts as an alternator dumping current back into the controller. For this purpose it is important that a bi-directional current sense amplifier be implemented to monitor and protect the motor as well as the controller.

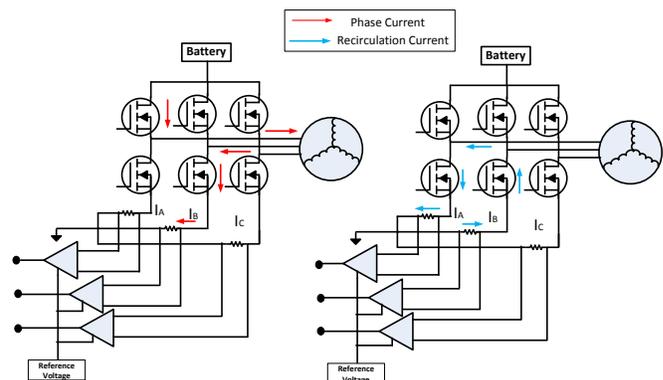


Figure 2. Varying Load Reference

Over Current Protection

One of the key features that is implemented in motor control circuitry is over current protection (OCP). In the system the output current from low-side is sampled by the ADC in the processor. If the processor detects the sampled output current has exceeded the threshold, the controller can be shutdown. While this is the simplest approach to achieve OCP the disadvantage with this implementation is the latency added by the ADC conversion. If faster protection is needed a dual comparator can be connected as shown in Figure 3. The two outputs of the comparator can easily be connected to the GPIO to trigger a shutdown command sequence or action when an alert is identified. One of the drawbacks of using the low-side sensing with dual comparator is the increase in the number of components needed to accomplish OCP.

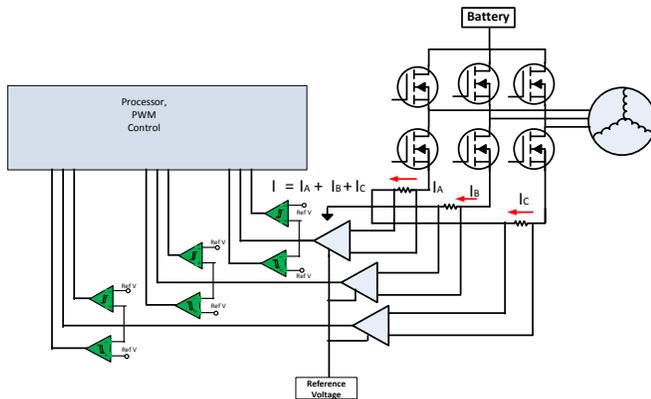


Figure 3. Discrete Current Sense Amplifiers And Comparators

The [INA303](#) includes a high common-mode, bi-directional current-sensing amplifier and two high-speed comparators configured to detect overcurrent conditions. The [INA303](#) comparators are in a window configuration. The device features an adjustable limit threshold range for each comparator set using an external limit-setting resistor. This current-shunt monitor can measure differential voltage signals on common-mode voltages that can vary from 0 V up to 36 V, independent of the supply. The open-drain alert outputs can be configured to operate in either a transparent mode (output status follows the input state) or in a latched mode (alert output is cleared when the latch is reset). The alert response time for comparator one is under 1 μs while the alert response for comparator two is set through an external capacitor ranging from 3 μs to 10s.

[Figure 4](#) describes the configuration of [INA303](#) in a low-side motor drive application for phase1. For phase2 and phase3 measurements two additional [INA303](#) will be required. The [INA303](#) has a maximum offset voltage of 35 μV and a drift of 0.5 $\mu\text{V}/^\circ\text{C}$. Low offset, drift and gain error enable accurate measurements across temperatures. With an output slew rate of 4V/ μs , the phase currents can be measured accurately at lower duty cycles with narrow pulses. A 1 μs delay on ALERT1 and an adjustable delay on ALERT2 pin from 3 μs to 10s enables optimization for various applications. The Analog output of [INA303](#) can be connected to the ADC of the processor. While the two comparator outputs can be connected to GPIOs of the processor. The threshold of the comparator1 can be set by RLIMIT1 resistor. The lower threshold for comparator2 can be set using RLIMIT2 resistor. This configuration can ensure that the motor and the controller can be protected against damage by ensuring the current remains within the safe operating region.

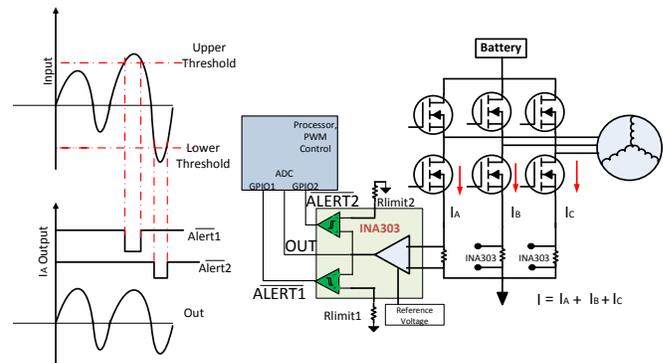


Figure 4. Low-Side sensing with [INA303](#)

Alternate device recommendations

The [INA300](#) is another recommended device if the system requires only an over current feature. [INA300](#) is a current sense comparator only. The [INA300](#) has an option to select multiple response times. The fastest available response time is 10 μs .

For applications requiring only a single over-current threshold the [INA301](#) is the recommended device

Similar to the [INA303](#), the [INA302](#) can be used for applications where two over-current alerts are needed. For example if independent threshold levels are needed for a warning condition as well as a critical fault condition, the [INA302](#) can be used. For applications that do not require the integrated comparator for on-chip over-current detection, use the [INA181](#).

Table 1. Alternate Device Recommendations

Device	Optimized Parameter	Trade-Off
INA300	Package	No analog output, slower response
INA301	Response time, Package	Single alert
INA302	Warning & Critical Alert Capability	Not configured as a window comparator
INA181	Package: SC70-6 & SOT23-6, Lower Cost	Amplifier only

Table 2. Related TI TechNotes

SBOA162	Measuring Current To Detect Out-of-Range Conditions
SBOA163	High-Side Motor Current Monitoring for Over-Current Protection
SBOA168	Monitoring Current for Multiple Out-of-Range Conditions
SBOA190	Low-Side Current Sense Circuit Integration
SBOA192	External Current Sense Amplifiers vs Integrated On-Board Amplifiers for Current Sensing

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated