

Extending Single Input Charger to Dual Input Applications

Mao Ye

PMP - Portable Power

ABSTRACT

This application report extends a single input charger IC to dual input (AC adapter and USB) applications. First, a low-cost linear charger IC (bq24080) example is presented, and a CFE (charger front-end) protection IC (bq243xx) is used to provide Li-ion battery safety protection from charging-system failures. Second, the bq24100 is given as another example for high-voltage, switch-mode charger applications. Finally, the bq24100 with power-path selection is presented for high-current application.

Today, many portable products such as cell phones, MP3 players, and PDAs (personal digital assistant), etc., use a single-cell Li-ion battery as their primary power source. In the past, only an AC adapter was used as the power source for charging the battery. This scenario remained unchanged until recently.

The USB (universal serial bus) is now becoming the most popular interface to connect peripherals to personal computers (PC). The USB not only can transfer data between portable devices and the host PC, but it also allows power transmission over the USB cable. As a result, it is feasible for a handheld product to charge its battery while it is connected to a host PC through the USB cable. Most of today's portable products can be powered from an AC adapter, a USB cable, or a Li-ion battery.

For dual input applications, charger integrated circuits (IC) that support dual inputs are the first choice for system designers and are now available with many unique features. However, for those charger ICs that only support a single input, a small auxiliary circuit can be added to extend these charger ICs to support dual input applications. This can save cost, printed-circuit board space, and engineering design time.

Among the single input charger ICs from Texas Instruments, the bq24080 and bq24081 are highly integrated and flexible Li-ion linear charge devices targeted at low-cost, space-limited charger applications. These devices act as stand-alone battery chargers up to a 1-A charge current and work in three phases: conditioning, constant current, and constant voltage. Charge is terminated based on minimum current. An internal timer provides a backup safety for charge termination.

Figure 1 shows a minimum component solution by using the bq24080 as a Li-ion battery charger. In this case, only four components including the bq24080 are required. The fast-charge current is set by a resistor on the ISET pin, while precharge current and termination current are 1/10th of the fast-charge current. The total charge timer typically is set to 7 hours and the precharge timer to 30 minutes.

To extend this charger to a USB input application, designers must follow the USB specification, which defines load current limits that a USB device can draw from the host. Three operating modes are allowed. First is the suspend mode, wherein the USB devices stand by and draw less than 500 μ A from the host. Second is the low-power mode, wherein the USB devices current can be up to 100 mA. Third is the high-power mode, wherein the current consumption can be as high as 500 mA.

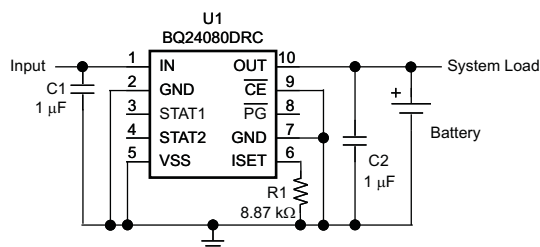


Figure 1. Minimum Component Count Li-Ion Battery Charger Using bq24080

The simplest and lowest cost solution to extend single input to dual inputs is adding two common-cathode Schottky diodes as shown in Figure 2(a). The two input voltages should not be presented at the same time. Otherwise, both diodes can be turned on and current is shared between two input terminals if the difference of two input voltages is less than the diode forward-voltage drop. When the difference is more than the diode forward-voltage drop, the higher voltage input powers the charger. The potential problem for this solution is the voltage drop across the Schottky diodes, which not only reduces system efficiency but also may cause battery charge problems when the USB bus voltage is too low. According to USB specification, the USB bus can be as low as 4.4 V, whereas the Schottky diode usually has a 0.2-V to 0.5-V forward-voltage drop for a 100-mA to 1-A range. Considering the charger IC internal dropout voltage, the voltage left for charging the battery may be lower than the voltage regulation set point, which is 4.2 V for most Li-ion batteries. As a result, in this situation, the battery cannot be fully charged.

To reduce the voltage drop across the Schottky diode, a P-channel MOSFET can be used to replace the Schottky diode as shown in Figure 2(b) and Figure 2(c). Figure 2(b) is a good trade-off between performance and cost. The body diode of the MOSFET acts as a Schottky diode initially to power the charger; then the proper FET is turned on to reduce the body diode forward-voltage drop and power dissipation. For example, in Figure 2(c), the gate of Q1 is connected to the adapter input and to ground by resistor R1. When the adapter is presented, the gate of Q1 is pulled high to turn off by adapter input voltage. When the adapter is not presented, the gate of Q1 is pulled to ground by resistor R1 to turn on Q1 if the USB is presented. Q2 and R2 perform the same function for adapter input. The gate resistor should be in the range 40 kΩ to 100 kΩ to meet the USB input impedance requirement.

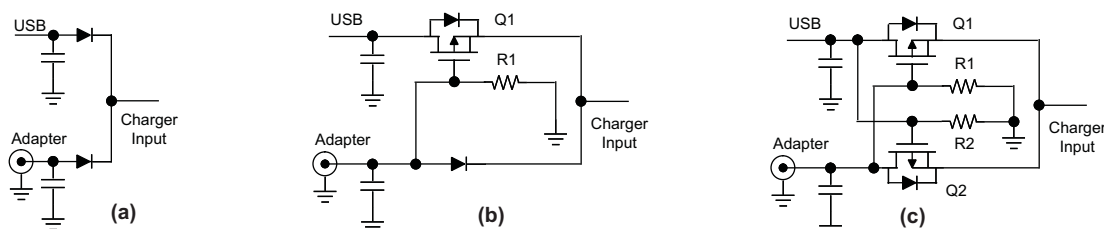


Figure 2. Typical Auxiliary Circuits for Dual Input Applications

The bq2408x charge IC has the current capability up to 1 A which is higher than USB 500-mA current limit. By adding some additional components to the ISET pin, the charger is capable of a higher charge rate from the AC adapter to a short fast-charge time.

Figure 3 shows an implementation of a dual input charger. Pulling up the \overline{CE} pin to high disables the charger to meet the USB suspend-mode requirement. R1 gives a default USB low-power mode, 100-mA charge current. Turning on Q1A adjusts the ISET pin resistance to get the USB high-power mode, 500-mA charge current. Q1B turns on if the AC adapter is present and changes the fast-charge current to 800 mA.



To provide safety protection for the Li-ion battery from failures of a charging system, Texas Instruments now has many options for charger front-end protection for IC products. An IC of the bq243xx family continuously monitors the input voltage, the input current, and the battery voltage. In case of an input overvoltage condition, the IC immediately clamps the voltage at its output to a safe value. If the overvoltage condition persists for more than a few microseconds, the IC removes power from the charging circuit by turning off an internal switch. In the case of an overcurrent condition, it limits the system current at the threshold value, and if the overcurrent persists, switches the pass element off after a blanking period. Similarly, if the battery voltage rises to unsafe levels while charging, power is removed from the system and there is no output from bq243xx. Additionally, the IC also monitors its own die temperature and switches off if it becomes too hot.



3

with a CFE protection IC. The 24.9-k Ω resistor connected to the ILIM pin gives a 1-A current limit set point. The 100-k Ω resistor between the VBAT pin and the battery positive terminal limits the current into the battery, if the CFE IC fails. The FAULT pin is in open-drain output status; when it is low, it indicates that the internal FET has been turned off due to input overvoltage, input overcurrent, or battery overvoltage.



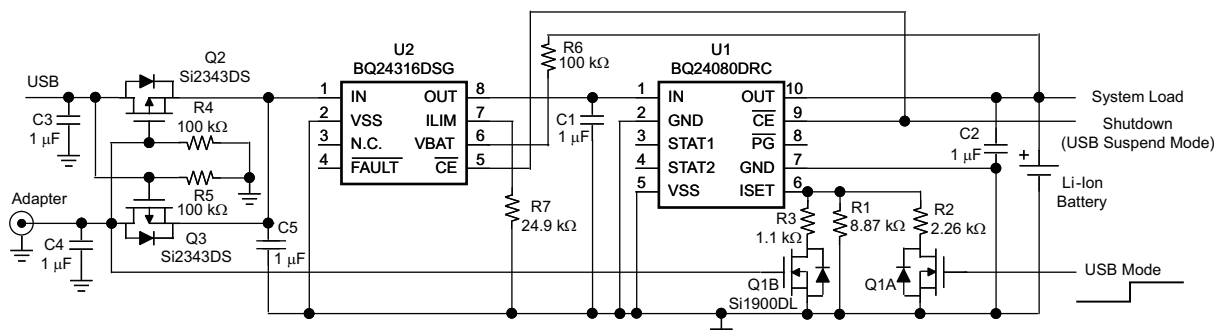


Figure 5. Dual Input Charger With CFE Protection IC


Figure 6 (a) and (c) shows USB and AC adapter hot plug-in waveforms, and (b) and (d) shows their zoom-in detail waveforms, respectively. The bq24316 has a 8-ms delay time to wait for input voltage stable. After 8 ms, the bq24316 turns on its internal FET to power up the charger IC. It is clear that the charger IC does not detect any overvoltage spike.

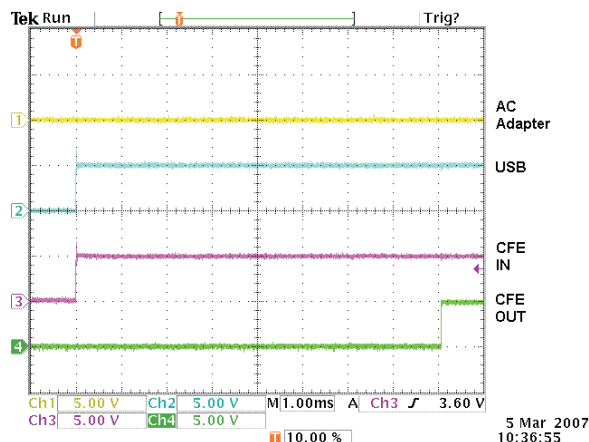


(a) USB Hot Plug-in

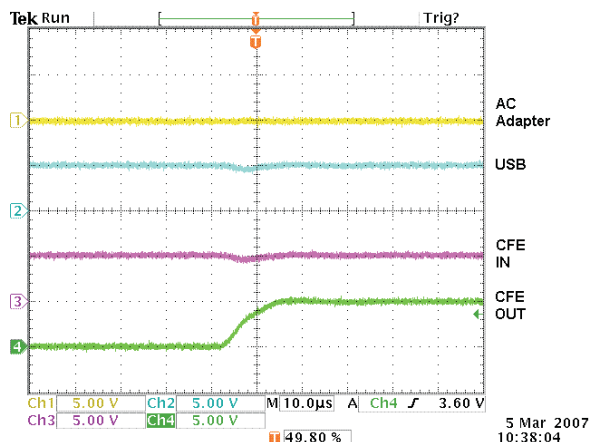

(b) USB Hot Plug-in Zoom-in

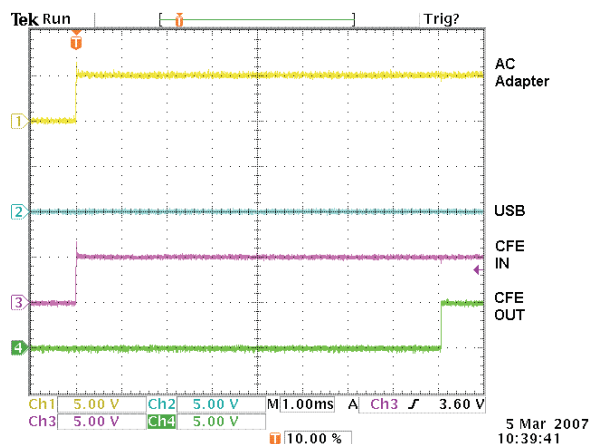


(c) AC Adapter Hot Plug-in

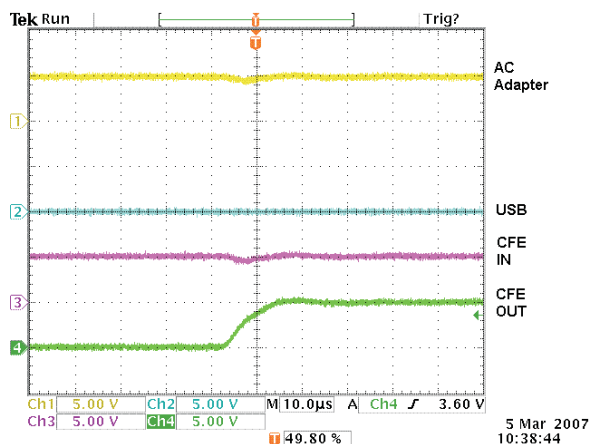

(d) AC Adapter Hot Plug-in Zoom-in

Figure 6. Hot Plug-in Waveforms With CFE Protection IC

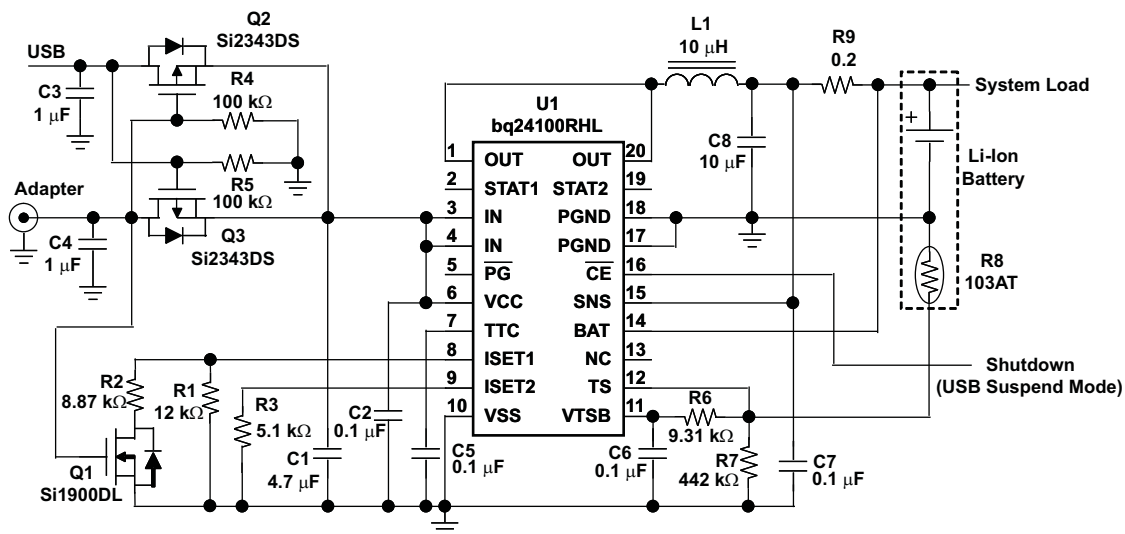For other power-path selection solutions, see the Texas Instruments application report *Implementations of Battery Charger and Power-Path Management System Using bq2410x/11x/12x (bqSWITCHER™)* (SLUA376).



5

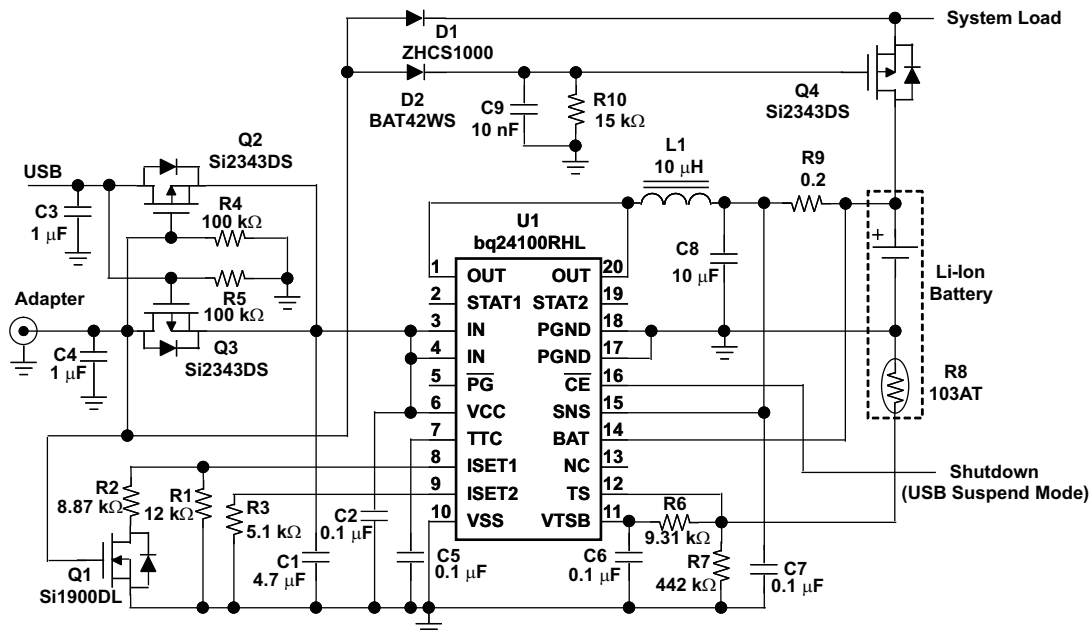


Figure 8. Dual Input Charger With Power Path Selection Solution

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2009, Texas Instruments Incorporated