

Achieving Different Charge Voltage for bq2408x

Mao Ye

PMP - BMS Battery Charge

ABSTRACT

By changing standard 4.2-V charge voltage to 4.1 V or lower, rechargeable lithium-ion (Li-Ion) battery cycle life can be extended at low temperature. New chemistry batteries such as the LiFePO_4 rechargeable battery requires a 3.6-V charge voltage. All these new applications need a nonstandard charge voltage. This application report gives examples of using the 4.2-V bq24085 charger to achieve different charge voltage.

The bq24085/6/7/8 series are highly integrated Li-ion and Li-polymer linear chargers, targeted at space-limited portable applications. The bq2408x series offers a variety of safety features and functional options, while still implementing a complete charging system in a small package. Multiple versions of this device family enable easy design in cradle chargers or in end equipment, while using low-cost or high-end ac adapters.

However, these linear chargers can only provide a standard 4.2-V charge voltage, while many of the new applications need a nonstandard charge voltage. For example, at low temperature, users prefer to reduce charge voltage to 4.1 V or lower to extend battery cycle life. The new chemistry battery, like the recently developed LiFePO_4 battery, needs 3.6 V instead of a 4.2-V charge voltage. This application report gives examples of using the 4.2-V bq24085 charger to achieve different charge voltage.

Figure 1 shows the circuit implementation to change charge voltage to 4.1 V when temperature is low. The bq24085 has an internal voltage reference of 4.2 V. This internal voltage reference is used for voltage loop control so that output voltage is regulated to 4.2 V. To change the output voltage, two resistors, R1 and R2, are used. The R1 and R2 values are selected so that the BAT pin is 4.2 V, whereas the OUT pin is 4.1 V. This requires a voltage source higher than 4.2 V connected to R2. R4 and the 4.7-V Zener diode Z1 are used for this higher voltage source. T1 is a PNP transistor used to control the voltage level switch from 4.2 V at normal temperature to 4.1 V at low temperature. R3 is the base bias resistor for T1. R3 and Z1 are connected to a host OC gate.

At normal temperature, the host OC gate is off. As a result, T1 is off so that R2 does not have an impact on regular charger operation. When temperature is low, the host turns on the OC gate to pull down R3 and Z1, so that R1 and R2 together provide feedback voltage to the BAT pin.

Assume that the input is 5 V and Z1 gives approximately 4.6 V, using the superposition principle gives the following equation.

$$V_{O(\text{REG})} = V_{\text{OUT}} \times \frac{R_2}{R_1 + R_2} + V_Z \times \frac{R_1}{R_1 + R_2},$$

Where $V_{O(\text{REG})} = 4.2 \text{ V}$, $V_{\text{OUT}} = 4.1 \text{ V}$, and $V_Z = 4.6 \text{ V}$.

Solving the equation gives the following answer:

$$R_2 = \frac{V_Z - V_{O(\text{REG})}}{V_{O(\text{REG})} - V_{\text{OUT}}} \times R_1 = \frac{4.6 - 4.2}{4.2 - 4.1} \times R_1 = 4R_1$$

Select $R_1 = 390 \text{ }\Omega$, then R_2 is 1.54 k Ω . Select $R_4 = 124 \text{ }\Omega$ to provide approximately a 3-mA bias current for Z1 at a 5-V input voltage. R3 can be a large resistor such as 133 k Ω to minimize bias current but not large enough to let T1 exit from the saturation state. Select the Z1 4.7-V Zener diode BZX84C4V7. Select the T1 15-V PNP transistor ZXT25015 which has very high gain so that the saturation voltage drop is only in the several mV range which can be ignored.

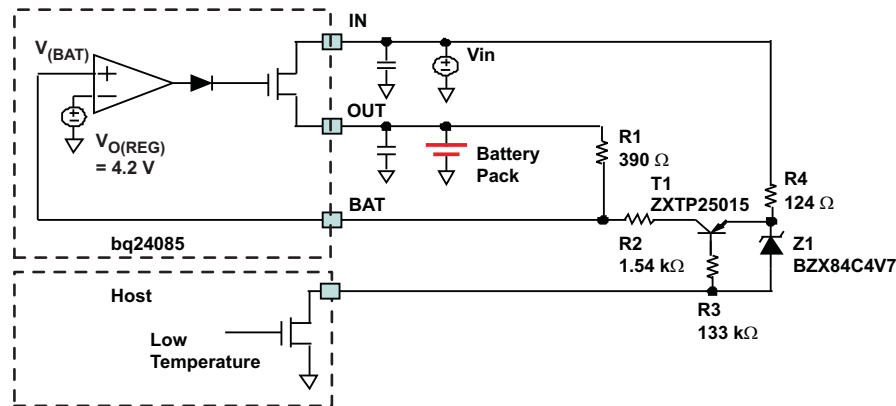


Figure 1. Circuit Implementation to Change Charge Voltage to 4.1 V by Using Zener Diode

Table 1 summarizes the test result. When input is changed from 4.5 V to 6.5 V, the output voltage is reduced from 4.163 V to 4.026 V, which is due to the Zener diode breakdown voltage change when bias current changes. If a very accurate voltage source (must be higher than 4.2 V) is available in the system, then connect this voltage source to the T1 emitter, and R4 and Z1 can be saved.

Table 1. Test Result of Zener Diode Circuit

V _{in} (V)	V _o (V)	V _z (V)	I _z (mA)
4.5	4.163	4.34	1.3
5	4.096	4.62	3.1
5.5	4.059	4.77	5.9
6	4.039	4.85	9.3
6.5	4.026	4.90	12.9

To improve the voltage regulation accuracy, an operational amplifier can be used to adjust the output voltage. **Figure 2** shows the circuit implementation to change the charge voltage to 4.1 V when temperature is low. At normal temperature, the host OC gate is off. As a result, U1 is a voltage follower that does not impact regulation voltage at 4.2 V. When temperature is low, the host turns on the OC gate to pull R1 down to ground; U1 is a noninverting amplifier. The output voltage regulation changes according to the following equation.

$$V_{OUT} = V_{O(REG)} \times \frac{R_1}{R_1 + R_2}$$

Where $V_{O(REG)} = 4.2$ V, $V_{OUT} = 4.1$ V

Solving the equation gives the following result.

$$R_1 = \frac{V_{OUT}}{V_{O(REG)} - V_{OUT}} \times R_2 = \frac{4.1}{4.2 - 4.1} \times R_2 = 41R_2$$

Select $R_1 = 10$ kΩ, then R_2 is 410 kΩ. Select standard 412 kΩ. Select U1 for low-power supply current with an extremely low input bias current operational amplifier such as TLV2241. **Table 2** summarizes the test result. When input is changed from 4.5 V to 6.5 V, the output voltage only changes 16 mV, which is much smaller than the Zener diode circuit.

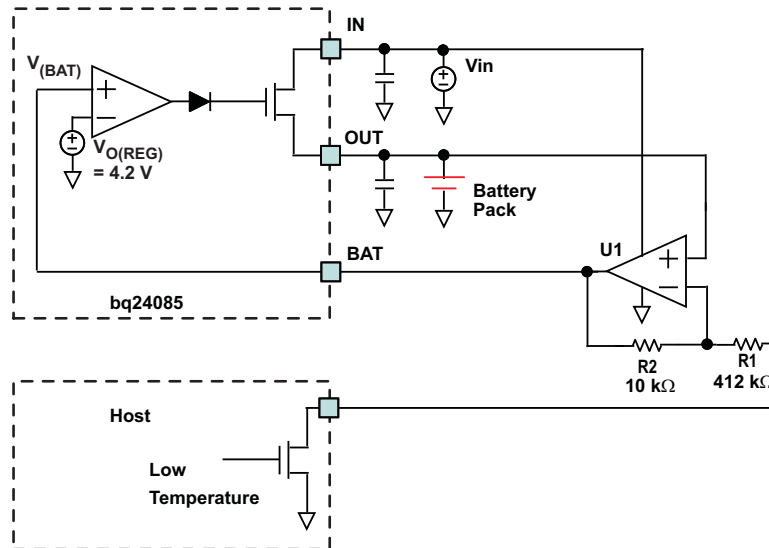


Figure 2. Circuit Implementation to Change Charge Voltage to 4.1 V by Using an Operation Amplifier

Table 2. Test Result of Operational Amplifier Circuit

V _{in} (V)	V _o (V)
4.5	4.117
5	4.101
5.5	4.102
6	4.102
6.5	4.103

A new chemistry battery, like the recently developed LiFePO₄ battery, needs 3.6 V instead of a 4.2-V charge voltage. A Zener diode solution is unsuitable because the voltage regulation variation is much higher than the 4.1-V case. As a result, the operational amplifier solution is used. The voltage regulation needs to be changed to 3.6 V at normal temperature by connecting R1 directly to ground. Figure 3 shows the circuit implementation to change the charge voltage to 3.6 V.

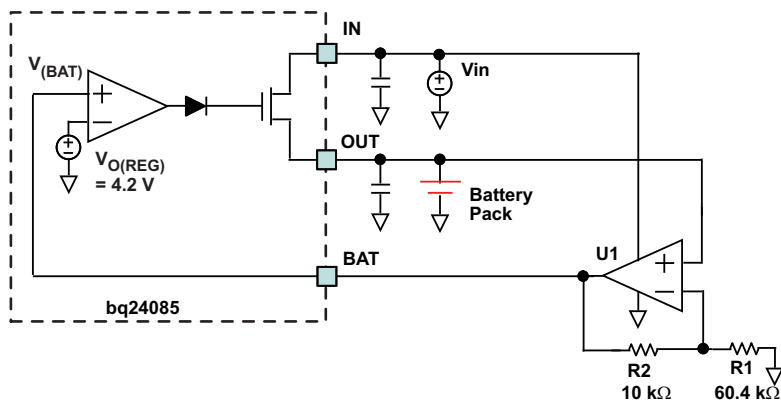


Figure 3. Circuit Implementation to Change Charge Voltage to 3.6 V by Using an Operational Amplifier

The output voltage regulation changes according to the following equation:

$$V_{OUT} = V_{O(REG)} \times \frac{R_1}{R_1 + R_2}$$

Where $V_{O(REG)} = 4.2 \text{ V}$, $V_{OUT} = 3.6 \text{ V}$

Solving the equation gives the following result.

$$R_1 = \frac{V_{OUT}}{V_{O(REG)} - V_{OUT}} \times R_2 = \frac{3.6}{4.2 - 3.6} \times R_2 = 6R_2$$

Select $R_1 = 10 \text{ k}\Omega$, then R_2 is $60 \text{ k}\Omega$. Select the standard $60.4 \text{ k}\Omega$. [Table 3](#) summarizes the test result. When the input is changed from 4.5 V to 6.5 V , the output voltage only changes 3 mV .

Table 3. Test Result of Operational Amplifier Circuit for 3.6-V Output

V _{in} (V)	V _o (V)
4.5	3.604
5	3.605
5.5	3.606
6	3.606
6.5	3.607

The two modification circuits both have a drawback. When a battery is removed, the output follows input, and Charge Done status is indicated. However, it is acceptable for those applications where the battery pack is unremovable.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2009, Texas Instruments Incorporated