

## NCP1650 Benchtop Assistance

Prepared by: Alan Ball  
ON Semiconductor  
Applications Engineer



ON Semiconductor®

<http://onsemi.com>

### APPLICATION NOTE

The NCP1650 is a high-performance, Power Factor Correction IC. It is capable of producing a high power factor input current waveform under continuous and discontinuous modes of operation. It is also a highly integrated device, and as such, requires fine tuning for optimum performance. The purpose of this application note is to assist in troubleshooting and fine tuning this circuit.

#### Troubleshooting

When troubleshooting this circuit, always use an oscilloscope. DVM readings will not show oscillations, spikes or other waveforms that may be helpful in determining the cause of the problem.

Be aware that this is a non-isolated power converter that is connected to a high-voltage, AC line. The ground of this circuit will be at an AC potential and could pose a shock hazard. **Use an approved isolation transformer** before connecting oscilloscopes or other test equipment to this circuit.

#### Output Does Not Regulate

1. High Output Voltage If the output voltage is greater than 8% of the level of the designed output voltage, check the voltage divider from the output to pin 6. Make sure that the resistor values are correct, and that the resistors are connected properly.
2. High Output Voltage If the output voltage is approximately 8% above the designed output level, the overvoltage comparator is controlling the loop. The switching will be erratic as the overvoltage comparator inhibits the operation of the loop.

The input to the error amplifier (pin 6) should be 4.3 volts under this condition. The output of the error amplifier (pin 7) should be high (approximately 6.0 volts). If it is not high, check connections to this node.

The voltage/power OR'ing network inverts this signal, which should cause the output of the reference multiplier (pin 4) to be approximately zero volts.

The averaged current signal on pin 10 of the current sense amplifier should be less than the output of the reference multiplier on pin 4.

3. Low Output Voltage If the output voltage is less than the designed output level, check the values in the output voltage divider that connects to pin 6 of the IC.

If the voltage divider values are correct, check the output of the power error amplifier at pin 8. If this voltage level is higher than the output of the voltage error amplifier (pin 7), the power circuit is limiting the output. Check to make sure that the load is within the rated range, and that the values of R10, R9, and the current shunt are correct.

#### Unit Does Not Start

1. Typically, the inability of this unit to start-up is due to inadequate Vcc. The NCP1650 requires a minimum of 10.5 volts to turn on, and 9.5 to maintain operation. If the Vcc voltage drops below 9.5 volts, the chip will shut down.

When the chip begins operation, the bias current will increase from a level of 0.5 mA to about 5.0 mA. Depending on the start-up circuit used, there may not be enough energy available to get the unit started before the Vcc drops below 9.5 volts.

In this case, a higher value Vcc cap may solve the problem, and/or a higher current start-up circuit.

If the start-up circuit is operating properly, check the voltage on pin 6. This pin has a shutdown feature that requires a voltage of greater than 0.75 volts for the chip to come out of its shutdown mode and commence operation.

#### Failure of Power Switch or High Voltage Diode


Overheating is the main cause of failures of these devices. The rectifier diode will experience significant heating due to the reverse recovery spike (unless a special circuit is used to reduce this effect). Measure the temperature of the package of both of these devices with a thermocouple and assure that they do not exceed the manufacturers ratings. Additional heatsinking and/or alternative parts may be required to keep the temperature in a safe range.

The power switch has several protection circuits within the NCP1650 controller. The main one being the instantaneous current limit. If peak current is a concern, check the values per the Excel spreadsheet or review the design equations in the data sheet.

The voltage on the power switch will exceed the output voltage by a diode drop plus any spikes that may occur. A good layout will keep these spikes to a minimum. Observe the drain pin of the power switch with a wide bandwidth oscilloscope to look for spikes. Spikes can be reduced by adding snubbers or modifying the layout to reduce path lengths between the inductor, drain and rectifier anode.

**Noise Problems**

Noise issues can be identified by abrupt changes in the current waveform. Instabilities will cause smooth oscillations, but noise will cause sharp edges as the current steps from one level to another.

 


**Figure 1. Example of Input Current Waveform Distortion Due to Noise Issues**


Possible causes are:

1. Poor grounding. In general, one of two grounding schemes should be used.
  - **Single Point Ground** – This is sometimes referred to as a “star ground”. All major power traces should be routed as close as possible to a single point, and routed directly to that point. This includes the shunt resistor, FET source, output capacitor, input bypass capacitor, and one trace going to all signal circuitry. The chip ground should be as close as possible to the ground side of the shunt resistor.
  - **Ground Plane** – One layer of the printed circuit board is left as a solid copper plane and all grounds are connected to this plane. Even with a ground plane, it is recommended to keep the high power grounds (as described in the above paragraph) close to each other, as well as keeping the chip ground close to the current shunt resistor ground.
2. Reduce rise and fall times of the power device. Increasing the resistance in the gate lead of the power FET will reduce the speed of its transitions. This will result in increased switching losses in the power switch. Snubber circuits can be added across the FET and/or diode to reduce noise levels. There are several types of snubbers including RC and RCD configurations.
3. Noise can also be radiated from various sources. The node of the FET drain, output rectifier, and boost inductor is a very noisy source, with both high voltages and high  $dv/dt$ 's. Sensitive components, which include most bias components of the NCP1650, should be kept away from this node. Traces between these components should be kept as short as possible to reduce these emissions.

**Performance**

 

**Figure 2. AC Ref with Phase Delay**

 

**Figure 3. AC Ref with Minimal Phase Delay**

### How to Improve Harmonics and Distortion

Low harmonic content and distortion are achieved by forcing the input current to exactly replicate the waveshape of the input voltage. To do this the output of the reference multiplier must be an accurate copy of the input haversine waveform. It is the function of the AC error amplifier loop to force the input current to copy this waveform. This loop includes the current sense amplifier averaged output, the AC error amplifier, and the output of the reference multiplier.

1. Check output of reference multiplier. With an oscilloscope, view the waveshape on pins 4 and 5. Pin 4 should copy the waveshape of pin 5. If not, confirm that the AC input (pin 5) does not exceed 4 volts peak, and check the output of the voltage error amplifier per the next step. The waveform on pin 5 (AC input) should be a scaled version of the input haversine after the rectifiers. If it is shifted in phase or does not go to zero, the cap on pin 5 should be reduced in value. Decreasing the value on pin 5 will reduce errors in the reference signal, but also increase the AC ripple (see Figures 2 and 3).
2. Check output of voltage error amplifier. It should be a DC signal. If there is much ripple on it, recheck calculations and components for the compensation network of C7 and R7. If the ripple is random, it could be a noise problem. Check grounding and proximity to high frequency, high voltage/current nodes. If the ripple is at the line frequency reduce loop bandwidth by modifying compensation components on pin 7. It is often helpful to add a small bypass capacitor to this point. Start with a value that is 1/100<sup>th</sup> of the value of C7.
3. Check average current signal on pins 10 and 11. There should be a small amount of switching frequency ripple (up to several hundred millivolts). If other frequencies are noted determine if it is a constant frequency. Random spacing of peaks indicates noise, repeatable spacing indicates an oscillation. If circuit is oscillating, reduce value of R3 and increase C3 by the same percentage.
4. If the voltage error amplifier and average current signal are both good, harmonics may be reduced by increasing the bandwidth of the AC error amplifier. To do this decrease the value of C3. Be cautious when doing so, to maintain loop stability. If there are oscillations on pins 10 and 11 (see Figure 4), reduce the gain of the current shaping loop by decreasing the value of R3 and increasing the value of C3 by the same percentage.

 


Figure 4. Current Shaping Loop Oscillations

### Poor Power Factor

Poor power factor is caused by two phenomena. One is the distortion of the input current waveform, relative to the input voltage waveform. The other is the phase shift of the input current waveform. Improving the harmonics and THD will improve the power factor due to distortion issues. The input EMI filter can cause poor power factor due to its capacitance, especially at high line.

The reason that the power factor suffers at high line is the phase shift due to the combination of the input current to the converter, and the current in the EMI capacitors. The input current to the converter reduces at high line, due to the fact that the unit is essentially a constant power device and as the line voltage increases, the line current must decrease proportionally. The capacitor current increases at high line due to the increased voltage on the capacitors. The following example illustrates this point.

For a 1000 watt unit, with an efficiency of 95%, and an input voltage range of 85 to 265 volts, the input current would be:

$$I_{in_{low}} = 1000 \text{ w} / (85 \text{ v} \times .95) = 12.4 \text{ amps}$$

$$I_{in_{high}} = 1000 \text{ w} / (265 \text{ v} \times .95) = 3.97 \text{ amps}$$

This current is in phase with the input voltage.

If we assume a total input capacitance of 8.0  $\mu\text{F}$ , and a line frequency of 60 Hz, the reactive current is:

$$I_{z_{low}} = 85 \text{ v} \times 2 \times \pi \times 60 \text{ Hz} \times 8.0 \mu\text{F} = .26 \text{ amps}$$

$$I_{z_{high}} = 265 \text{ v} \times 2 \times \pi \times 60 \text{ Hz} \times 8.0 \text{ } \mu\text{F} = .80 \text{ amps}$$

The power factor due to the phase displacement is:

$$Q_{low} = \arctan (.26/12.4) = 1.20^\circ$$

$$PF_{low} = \cos Q = 1.00$$

$$Q_{high} = \arctan (.80/3.97) = 11.4^\circ$$

$$PF_{high} = \cos Q = .980$$

It is recommended that the AC caps be kept as small as possible, while still assuring proper operation, as well as meeting the EMI specifications. One criteria to consider is the value of the capacitance on the AC side of the line vs. the value on the rectified side.

The capacitor on the rectified side of the line, will have a DC component associated with it. It should also carry the majority of the high frequency switching current, as opposed to requiring it to flow through the rectifiers.

A good starting point is to calculate the allowable high-frequency voltage ripple for this capacitor. The input current will normally be in the continuous conduction mode of operation at low line and full load. The ripple on the input filter capacitor due to this waveform is:

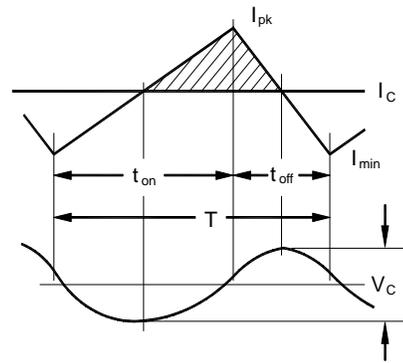


Figure 5. Input Capacitor Voltage and Current Waveforms

$$V_C = \frac{\Delta I}{8 \cdot C} T$$

Where:

V<sub>C</sub> is the capacitor peak-to-peak voltage in volts

ΔI is the peak-to-peak ripple current. This can be found on sheet 1 of the NCP1650 design spreadsheet in the “P-P Ripple Current vs. Angle” graph.

T is the switching period in seconds

C is the capacitance in Farads

The capacitor on the AC side of the line should be at least a factor of 2 greater than the capacitor on the rectified side of the line and typically a factor of 5 or more. The capacitor on the rectified side of the line will tend to hold up the voltage at zero crossings, and will contribute to the distortion in the current waveform, whereas, the capacitor on the AC side of the line will help to filter any distortion at the zero crossings, but will cause phase shift.

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. “Typical” parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including “Typicals” must be validated for each customer application by customer’s technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer.

**PUBLICATION ORDERING INFORMATION**

**Literature Fulfillment:**

Literature Distribution Center for ON Semiconductor  
 P.O. Box 5163, Denver, Colorado 80217 USA  
**Phone:** 303-675-2175 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 303-675-2176 or 800-344-3867 Toll Free USA/Canada  
**Email:** ONlit@hibbertco.com

**N. American Technical Support:** 800-282-9855 Toll Free USA/Canada

**JAPAN:** ON Semiconductor, Japan Customer Focus Center  
 4-32-1 Nishi-Gotanda, Shinagawa-ku, Tokyo, Japan 141-0031  
**Phone:** 81-3-5740-2700  
**Email:** r14525@onsemi.com

**ON Semiconductor Website:** <http://onsemi.com>

For additional information, please contact your local Sales Representative.