

NCN5120 - Driving Relays in an Efficient Way



ON Semiconductor®

<http://onsemi.com>

APPLICATION NOTE

INTRODUCTION

NCN5120 is a receiver-transmitter IC suitable for use in KNX® twisted pair networks (KNX TP1-256). It supports the connection of actuators, sensors, microcontrollers, switches or other applications in a building network.

NCN5120 handles the transmission and reception of data on the bus. It generates from the unregulated bus voltage stabilized voltages for its own power needs as well as to power external devices, for example, a microcontroller.

NCN5120 assures safe coupling to and decoupling from the bus. Bus monitoring warns the external microcontroller for loss of power so that critical data can be stored in time.

NCN5120 has several voltage regulators to generate different voltages. One of these voltage regulators is a 20 V low drop linear regulator typically used for driving relays. Because NCN5120 has a high efficient adjustable DC-DC converter, driving of relays can be done in a more efficient way. This application note describes how to use the adjustable DC-DC converter for driving relays in an efficient way under all operating conditions.

STANDARD RELAY APPLICATION

Figure 1 gives the block diagram of the relay driving principle as used in KNX relay actuators today. A 20 V LDO is used to power the relays. Because 12 V relays are generally used, this 20 V needs to be converted down to 12 V. To minimize the required power to drive the relays, bistable relays are used which are controlled by H-bridges. The H-bridges itself are controlled by a microcontroller (microcontroller not displayed in Figure 1). Although bistable relays are used still a relatively high current is required to change the state of the relays. This current cannot be requested from the 20 V LDO because this would result in a too high current taken from the KNX bus. To make sure not too much current is sourced from the KNX bus a current limit circuit is added. A big storage capacitor (10 mF or higher) is used to store the energy required to drive the relays. Every time the relays are activated the voltage on the big storage capacitor will drop. Recharging of this capacitor will be relatively slow (due to the current limiter) but

because these relays are not operated at a very high rate this approach works perfectly.

NCN5120 RELAY APPLICATION

The 20 V LDO is not an efficient regulator to be used. NCN5120 has an adjustable DC-DC converter which is high efficient (DC2). One could decide to use DC2 to drive the relays. However, due to some limitations of NCN5120 this DC2 voltage could drop too much under certain situations (mainly when the capacitor needs to be charged). This would result in a too low voltage to drive the relays. Also, to store as much as possible energy in the big storage capacitor it's advised to have an as high as possible voltage.

Figure 2 gives the schematic for driving relays with DC2 and assures a stable voltage under all situations. Figure 3 displays only the DC2 part (which gives a more clear view on the operation).

With exception of DC2, the schematic as given in Figure 2 is very basic (see also NCN5120 datasheet). The connection between the KNX bus (see connector A and B) and NCN5120 makes use of all the standard components as given in the datasheet. A standard 16 MHz crystal is used and a clock signal is supplied back to the microcontroller (uC CLK). It's not mandatory to work in this way. The relay driving principle will also work when the microcontroller supplies the clock to NCN5120. RESETB and SAVEB are supplied to the microcontroller for monitoring of the status. A standard UART interface is used as communication between microcontroller and NCN5120 but any of the other interfaces will also do. DC1 is used as normal. FANIN/WAKE-pin is pulled to ground. Although this is not necessary, it's advised to do this. When FANIN/WAKE-pin is pulled to ground, more power can be taken from the KNX bus to recharge the big buffer capacitor faster (C₁₃ in Figure 2). V20V is not used in Figure 2 because we use DC2 to drive the relays.

Table 1 gives the components list for all required DC2 components. All components from Figure 2 which cannot be found back in Table 1 can be found back in the NCN5120 datasheet.

20 V LDO

Optional Current Limiter

20 V to 12 V

H-bridge

Relay 1

H-bridge

Relay 2

H-bridge

Relay 3

...

H-bridge

Relay n

The schematic diagram illustrates the NCN5120 microcontroller and its associated components. The microcontroller is a 40-pin device with the following connections:

- Power and Ground:**
 - VDDA (39) is connected to a 3.3V supply through capacitor C5.
 - TESTOUT (39) is connected to a 3.3V supply.
 - FANINWAKE (38) is connected to a 3.3V supply.
 - RESETB (37) is connected to a 3.3V supply.
 - SAVEB (36) is connected to a 3.3V supply.
 - XTAL1 (35) and XTAL2 (34) are connected to a crystal X1.
 - XSEL (33) is connected to a 3.3V supply.
 - XCLK (32) is connected to a 3.3V supply.
 - VSSD (31) is connected to ground.
 - VDDD (30) is connected to a 3.3V supply through capacitor C6.
 - VBUS2 (2) is connected to a 3.3V supply.
 - VBUS1 (6) is connected to a 3.3V supply.
 - VFILT (9) is connected to a 3.3V supply.
 - V20V (10) is connected to a 3.3V supply.
 - VDD2MV (11) is connected to a 3.3V supply.
 - VDD2MC (12) is connected to a 3.3V supply.
 - VSS2 (13) is connected to ground.
 - VSW2 (14) is connected to a 3.3V supply.
 - VIN (15) is connected to a 3.3V supply.
 - VSW1 (16) is connected to a 3.3V supply.
 - VSS1 (17) is connected to ground.
 - VDD1 (18) is connected to a 3.3V supply.
 - VDD1M (19) is connected to a 3.3V supply.
 - V20V (20) is connected to a 3.3V supply.
- Signal and Control:**
 - TXO (3) is connected to a 3.3V supply.
 - CCP (4) is connected to a 3.3V supply.
 - CAV (5) is connected to a 3.3V supply.
 - CEQ1 (7) and CEQ2 (8) are connected to a 3.3V supply.
 - SCK/UC2 (29) is connected to a 3.3V supply.
 - SDO/TXD (28) is connected to the Tx pin.
 - SDI/RXD (27) is connected to the Rx pin.
 - CSB/UC1 (26) is connected to a 3.3V supply.
 - TREQ (25) is connected to a 3.3V supply.
 - MODE2 (24) is connected to a 3.3V supply.
 - MODE1 (23) is connected to a 3.3V supply.
 - NC (22) and NC (21) are connected to ground.
- Other Components:**
 - Diodes D1, D2, and D3 are connected to the power supply lines.
 - Capacitors C1, C2, C3, C4, C8, C9, C10, C12, and C13 are connected to the power supply lines.
 - Resistors R1, R2, R4, R5, R6, R7, and R8 are connected to the power supply lines.
 - Inductor L1 is connected to the power supply line.
 - Inductor L2 is connected to the power supply line.
 - Transistor T1 is connected to the power supply line.

2

AND9149/D

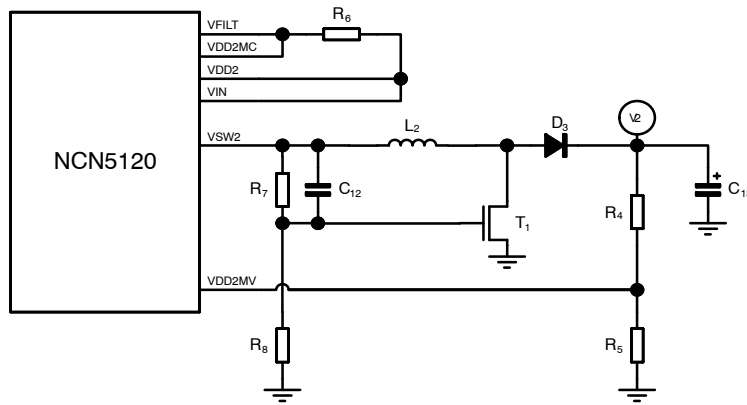


Figure 3. DC2 Schematic for Driving Relays

Table 1. DC2 BOM

Comp.	Value	Tolerance	Remarks	Notes
C ₁₂	56 pF	±10%		1
C ₁₃	12 mF	±20%		2, 4
D ₃	MBR1H100SFT3G		ON Semiconductor	
L ₂	220 μF	±10%	Coils Electronic DA54NP-221K	
R ₄	39 kΩ	±5%	0.0625 W	4
R ₅	10 kΩ	±5%	0.0625 W	4
R ₆	2.7 Ω	±1%	0.0625 W	3, 4
R ₇ , R ₈	100 kΩ	±1%	0.0625 W	
T ₁	2N7002LT1G		ON Semiconductor	

1. It's advised to take this value as close as possible to the input capacitance of T_1 .
2. The value of this capacitor will depend on the required energy for driving the relays.
3. R_2 (see Figure 2) should be lower than R_6 !
4. See below for defining the value.

R_4 and R_5 can be calculated as next:

$$R_4 = \frac{R_5 \times R_{VDD2M}}{R_5 + R_{VDD2M}} \times \frac{V_2 - 3.3}{3.3}$$

The current limiting resistor R_6 can be calculated as next:

$$R_6 = \frac{V_{OC}}{\sqrt{\frac{2 \times I_{FILT} \times T}{L_2 \left(\frac{1}{V_{FILT}} + \frac{1}{V_2} \right)} - \frac{V_{FILT} \times t_{del}}{L_2}}}$$

where:

- $VOC = 0.15$ (0.165 worst case)
- I_{FILT} = the maximum V_{FILT} current
- V_{FILT} = V_{FILT} voltage when relays are active (advised value is 12 V)
- $T = 4$ (5 worst case)
- L_2 = inductance of DC2 (in μH)

- V_2 = output voltage when relays are active (advised value is 13 V or 14 V)
- $t_{del} = 0.15$ (0.25 worst case)

The capacitor C_{13} can be calculated as next:


$$C_{13} = \frac{n \times i_{\text{relay}} \times t_{\text{act}}}{V_{\text{drop}}}$$

where:

- n = number of relays that are switched simultaneously
- i_{relay} = current required by one relay (V_2 / R_{relay} gives a good estimation)
- t_{act} = activation time of the relays
- V_{drop} = the allowed drop on V_{OUT}

A calculator is provided on the ON Semiconductor website as a guide for defining the optimum values (<http://www.onsemi.com/PowerSolutions/supportDoc.do?type=tools&rpn=NCN5120>).

KNX and the KNX logos are registered trademarks of KNX and its suppliers or licensors.

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of SCILLC's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada

Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910

Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com

Order Literature: <http://www.onsemi.com/orderlit>

For additional information, please contact your local
Sales Representative