

19 V, 3.0 A Universal Input AC-DC Adaptor Using NCP1271

Prepared by: Jon Kraft and Kahou Wong
ON Semiconductor



ON Semiconductor®

<http://onsemi.com>

APPLICATION NOTE

INTRODUCTION

The NCP1271 is one of the latest fixed-frequency current-mode PWM switching controllers with (1) adjustable Soft-Skip™ standby operation for low-level audible noise, (2) integrated high-voltage startup for saving standby power, (3) timer based overload fault detection, and (4) internal latch protection features. Table 1 summarizes all the features of an NCP1271 based power supply.

This application note presents an example circuit (Figure 1) using the NCP1271 (65 kHz version) in a flyback topology. The design steps and subsequent measurements are also included. An Excel based design worksheet is available at www.onsemi.com.

The measurements show that the 19 V, 3.0 A circuit delivers above 85% across a universal input (85 to 265 Vac). The no load standby consumption is 83 mW at 230 Vac and the light load operation is greater than 75% efficient.

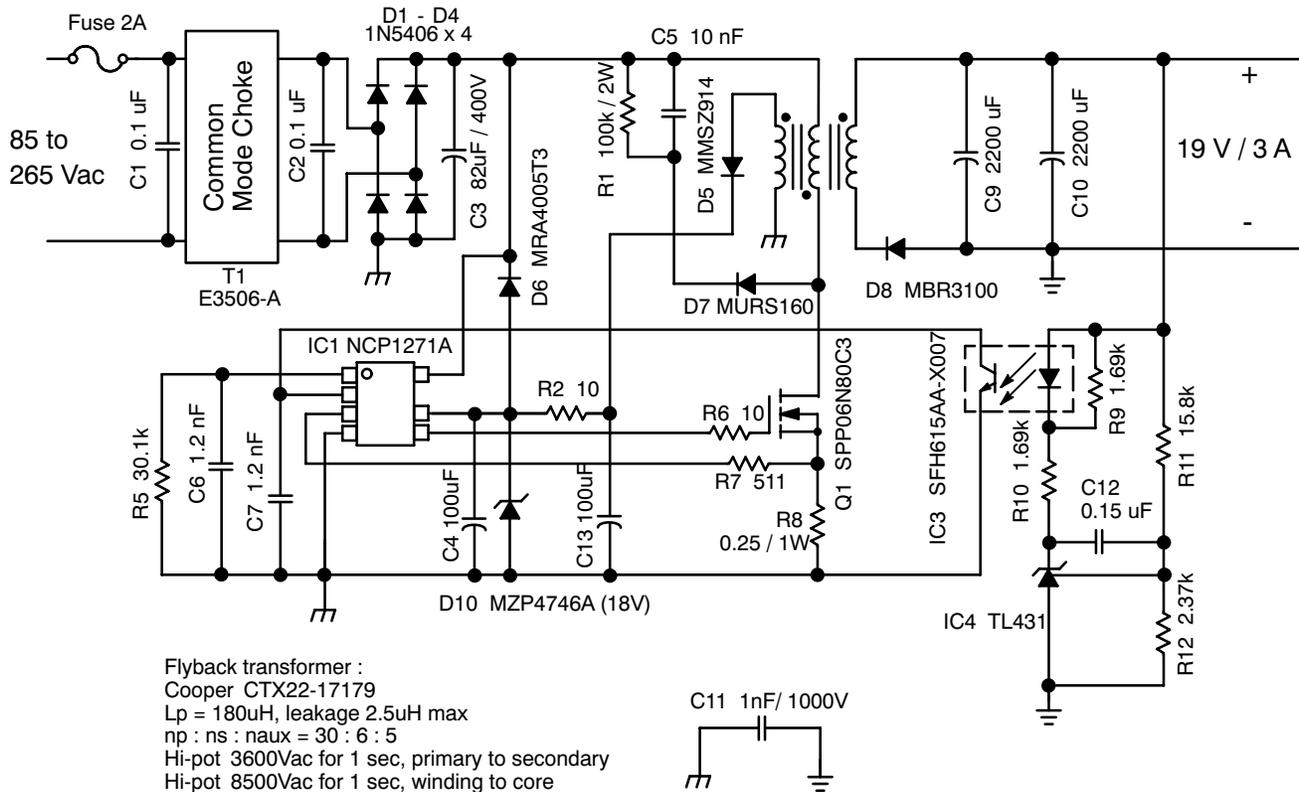


Figure 1. Application Circuit Schematic

Table 1. Features of Power Supply Using NCP1271

| | Operation Mode | Features |
|----------------------------|-----------------------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| Topology | CCM/DCM Flyback | <ul style="list-style-type: none"> Fixed-frequency current-mode control with inherent primary current limitation. Frequency jittering to soften the EMI signature. Built-in soft-start. Output short-circuit fault detection independent of the auxiliary winding. Integrated high voltage startup that minimizes standby power loss. |
| Standby Condition | Soft-Skip Operation | <ul style="list-style-type: none"> Adjustable skip level for optimal standby power consumption. Proprietary Soft-Skip to reduce the risk of low-frequency audible noise. Soft-Skip operation is automatically disabled if an abrupt transient load is applied from standby operation. This improves the output response to a transient load. |
| Fault Condition | Double Hiccup Restart | <ul style="list-style-type: none"> Double Hiccup operation minimizes the power dissipation in a fault mode and allows the application to auto-recover when the fault is removed. |
| Latch Protection Activated | Latch Off | <ul style="list-style-type: none"> An internal latch makes it easy to add overtemperature protection (OTP) or overvoltage protection (OVP) to any applications. Latch is reset by unplugging the AC input and allowing V_{CC} to drop below 4 V (typ). |

The Demo Board Specification

| | |
|----------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| Input | 85 to 265 Vac, 50 Hz |
| Output | 19 Vdc, 3.0 A, Isolated |
| Features | <ul style="list-style-type: none"> < 100 mW Input Power at 230 Vac Excellent Light Load Performance No Audible Noise > 85% Full Load Efficiency Short Circuit Protection Activates at < 100W for Any Input Voltage |

A Discontinuous Conduction Mode (DCM) flyback was selected for this application. DCM gives very good stability, small inductor size (lower leakage inductance), and good transient response.

Flyback Calculations

Several resources are available at www.onsemi.com to calculate the necessary component values for a flyback supply. In particular, an Excel based design spreadsheet can be found at:

www.onsemi.com/collateral/NCP1271SHEET.xls

Additionally, most of the other NCP12xx application notes also apply to the NCP1271. For detailed information on designing a flyback power supply, please visit AND8076/D. Other app notes which may also aid in the design include:

| | |
|-----------|--------------------------------------------------------------|
| AND8069/D | Tips and Tricks to Build Efficient Circuits With the NCP1200 |
| AND8205/D | How to Choose a Switching Controller for Design |
| AND8023/D | Implementing the NCP1200 in Low-Cost AC/DC Converters |
| AND8032/D | Conducted EMI Filter Design for the NCP1200 |
| AND8076/D | A 70 W Low Standby Power Supply with the NCP12xx Series |

Based on the results from the NCP1271 design spreadsheet, the final values for this adapter’s key flyback parameters were calculated to be:

- $N_p:N_s = 5:1$
- $L_p = 180 \mu\text{H}$
- $R_{CS} = 0.3 \text{ Ohms}$
- $I_{\text{peak}}(\text{full load}) = 3.5 \text{ A}$
- Switch Rating = 6 A, 800 V
- Diode Rating = 3 A, 100 V
- $R_{\text{snubber}} = 100 \text{ k}\Omega$
- $C_{\text{snubber}} = 10 \text{ nF}$

Setting the Short Circuit Protection Level

The current sense resistor (R_{CS} or R8), provides two functions. First it senses the primary current for current-mode PWM operation. Secondly, it provides the maximum primary current limitation according to equation 1:

$$I_{p(\text{max})} = \frac{1 \text{ V}}{R_{CS}} \quad (\text{eq. 1})$$

The short circuit protection activates when the $I_{p(\text{max})}$ current is reached for more than 130 ms (typ). This also corresponds to V_{FB} being greater than or equal to 3 V for 130 ms. Therefore, R_{CS} must be set large enough to ensure that the required peak current can always be delivered, but small enough to meet the short circuit protection requirements. A DCM flyback converter has the following relationship:

$$P_{\text{out}} = 1/2 \times L_p \times I_p^2 \times F_{\text{SW}} \times \eta \quad (\text{eq. 2})$$

Therefore, for an assumed efficiency of 80%, a peak current of 4 A should trigger the short circuit protection circuitry at 80 W. This corresponds to an R_{CS} value of 0.25 Ω . This change in R_{CS} may also require that the snubber and transformer be re-calculated to handle this level of peak current during the short circuit fault time. A few iterations of the Excel based NCP1271 design spreadsheet should produce a good starting point for the application’s design.

Over Power Compensation

For this demo board, the short circuit protection is activated with an output load of 76 W at 85 Vac and 93 W at 265 Vac. The variation in short circuit power level with

input voltage is due to the propagation delay (T_{prop}) of the NCP1271. This propagation delay has a more pronounced effect on the power delivered at high line than at low line as shown in Figure 2.

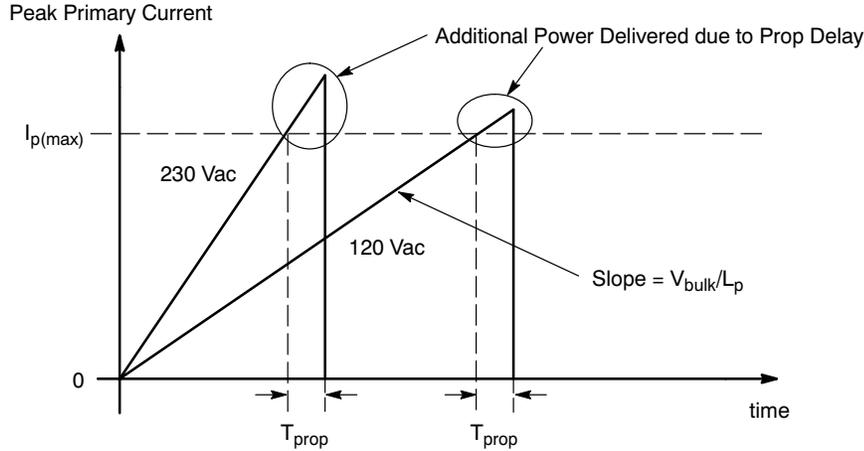


Figure 2. Effect of Propagation Delay on the Maximum Power Delivered at High Line and Low Line

This effect is called “Over Power” because it delivers more power than what is requested by the feedback loop. Specifically, for a DCM flyback system, the total power delivered to the output including the prop delay effect is:

$$P_{out} = \frac{1}{2} \cdot L_p \cdot (I_p(max) + V_{bulk}/L_p \cdot T_{prop})^2 \cdot F_{sw} \cdot \eta \quad (eq. 3)$$

The NCP1271 has been designed with a very low T_{prop} (50 ns typ). This minimizes the over power effect. However, if reduced variation is required, then over power compensation can be easily implemented by using one of the circuits shown in Figures 3 and 4.

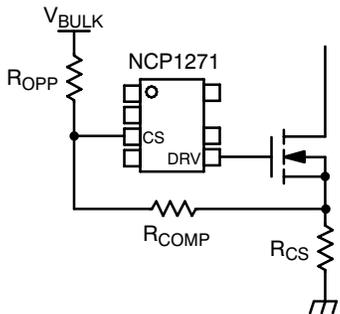


Figure 3. Over Power Compensation by means of a Resistor to the Bulk Voltage

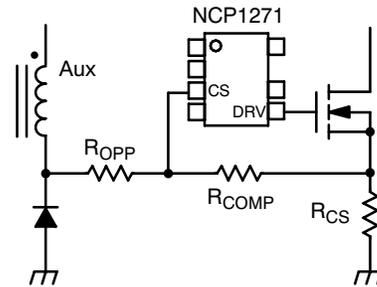


Figure 4. Over Power Compensation by Modifying the Auxiliary Winding Topology

The circuit in Figure 3 simply modifies the CS setpoint proportional to the HV bulk level. This creates an offset which compensates for the propagation delay. However, this does increase the standby power dissipation. Figure 4 gives another option which results in much lower power dissipation. By altering the position of the Aux winding diode, a new point is created whose voltage is proportional to V_{in} . The power dissipation is now reduced by a factor of $(N_p:N_{aux})^2$. Values for R_{opp} are best found experimentally to give suitable precision for the activation of the short circuit protection.

Biasing the Controller

The NCP1271 includes a high voltage (HV) startup pin (Pin 8) which charges V_{CC} to its operating level. This pin can be directly connected to the high voltage DC bus. Once the device is powered up, an auxiliary winding powers V_{CC} as shown in Figure 5.

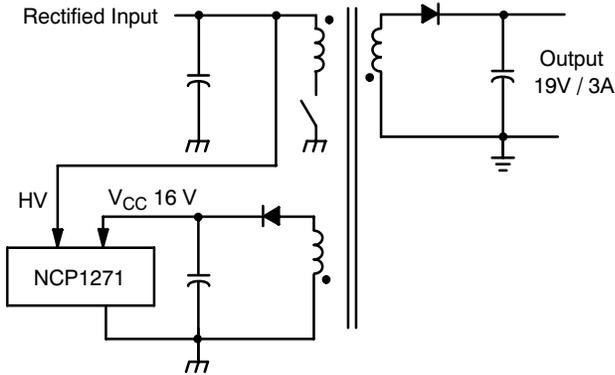


Figure 5. V_{CC} Biasing Scheme

The range of V_{CC} is from 10 V (min) to 20 V (max). Therefore, the auxiliary winding should be designed to give a level of V_{CC} within this range over all output loads. When the circuit is in standby mode, very few pulses are delivered and the auxiliary level decreases. To provide enough voltage range, a nominal V_{CC} level of 16 V was selected for this application. Additionally, an 18 V ($\pm 5\%$) Zener diode was added externally to protect the controller from abnormally high auxiliary levels. The 16 V bias supply is constructed from a 6:5 turns ratio (19 V:16 V) between the main output and the auxiliary winding.

Figure 6 shows the auxiliary supply circuit. A resistor is included to provide the flexibility to redesign the circuit for higher output voltages. Any extra bias voltage greater than 18 V is simply dissipated across the resistor.

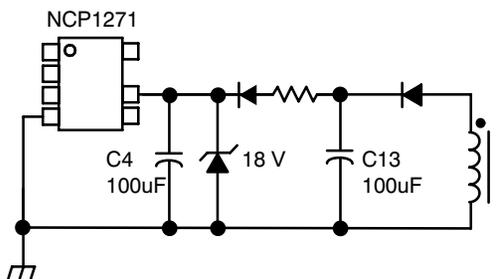


Figure 6. Auxiliary Supply

Soft-Skip Adjustment

When the load current drops, the compensation network responds by reducing the peak current. When the peak current reaches the skip peak current level, the NCP1271 enters skip operation to reduce the power consumption. The peak current level at which skip is entered should be set high for good standby power dissipation. However, it also needs to be set low enough that no audible noise occurs during each

bunch of skip pulses. To address this need, the NCP1271 has a proprietary Soft-Skip feature which ramps each bunch of pulses. This dramatically lowers acoustic noise and allows a higher skip level to be set for greater power savings. The NCP1271 also allows the designer to select the optimal level of the peak current during skip through a simple resistor from pin 1 to GND. This skip resistor sets the skip level according to equation 4:

$$V_{\text{skip}} = I_{\text{skip}} \times R_{\text{skip}} \quad (\text{eq. 4})$$

where $I_{\text{skip}} = 43 \mu\text{A}$ (typ)

The peak current when skip mode is activated can be calculated with equation 5:

$$I_{\text{peak(skip)}} = \frac{V_{\text{skip}}}{3V} \times I_{\text{peak(max)}} \quad (\text{eq. 5})$$

For this demo board, V_{skip} was set to 1.3 V ($R_{\text{skip}} = 30.1 \text{ k}\Omega$). And $I_{\text{peak(max)}}$ is $1 \text{ V} / 0.25 \Omega = 4 \text{ A}$. Therefore, $I_{\text{peak(skip)}} = 1.7 \text{ A}$.

Minimum On Time Limitation

The NCP1271 includes a current sense (CS) Leading Edge Blanking (LEB) filter. The LEB filter blanks out the first 180 ns (typ) of the CS voltage at the beginning of each drive pulse. This helps to prevent a premature reset of the output due to noise. However, this also results in a minimum on time of the device. The duration is equal to the LEB time (180 ns typical) and the propagation delay of logic (50 ns typical). If the application circuit is configured for 0% skip (by connecting Pin 1 to Ground), then that minimum on time duration may result in an abnormally high output voltage during no load conditions. Therefore, it is recommended to set skip to some small value rather than disable it completely.

Ramp Compensation

The NCP1271 also incorporates a feature called “ramp compensation.” Ramp compensation is a known mean to cure subharmonic oscillations. These oscillations take place at half the switching frequency and occur only during continuous conduction mode (CCM) with a duty-cycle greater than 50%. To prevent these oscillations, one usually injects between 50 and 75% of the inductor down slope into the CS pin. The NCP1271 generates an internal current ramp that is synchronized with the clock. This current ramp is then routed to the CS pin.

Since the flyback design in this app note is well within DCM operation, ramp compensation is not necessary. However, for designs that do run in CCM with the NCP1271, ramp compensation is easy to implement. It only requires one external resistor between R_{cs} and the CS pin. The value of the ramp resistor to obtain 50% inductor down slope injection can be calculated with the following equation:

$$R_{\text{ramp}} = 0.50 \times R_{\text{CS}} \times \frac{(V_{\text{out}} + V_f) \times \frac{N_p}{N_s}}{(L_p \times F_{\text{sw}} \times \frac{100 \mu\text{A}}{0.80})} \quad (\text{eq. 6})$$

Maximum Duty Cycle and Ramp Compensation

If the ramp resistor is set too high, the maximum duty cycle will be reduced. But as long as R_{ramp} is below 10 k Ω , this will not be a problem. A typical graph of the maximum duty cycle versus R_{ramp} is shown in Figure 7. However, it is not recommended to try to reduce the maximum duty cycle by the R_{ramp} value because this relationship is not guaranteed by the production tests of the device.

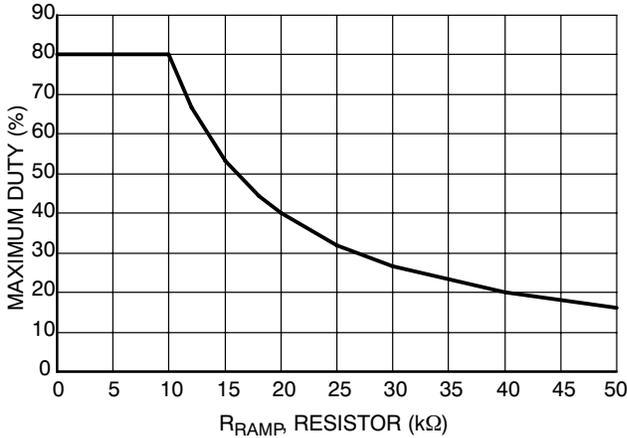


Figure 7. Maximum Duty Cycle Characteristics

Optional Output OVP Latch

The NCP1271 includes a feature where if Pin 1 is brought above 8.0 V (typ), the part will safely latch off the controller. The controller is reset by unplugging the AC input. This allows for easy implementation of overvoltage (OVP) or overtemperature (OTP) protection.

In order to pull the Pin 1 voltage above the latch threshold, a greater than 8.0 V source is needed. That is usually the bias supply voltage V_{CC} . Therefore, to protect Pin 1, a resistor (R_{limit}) is connected to limit the current below the maximum allowed level. In addition, the internal ESD diode will limit the maximum voltage on Pin 1 to about 10 V.

This latch off feature can be configured in a variety of ways. Some of the most popular include using the auxiliary winding to detect an overvoltage and using an NTC resistor to detect an overtemperature condition. A few variations of these circuits are listed in Figures 8 to 11.

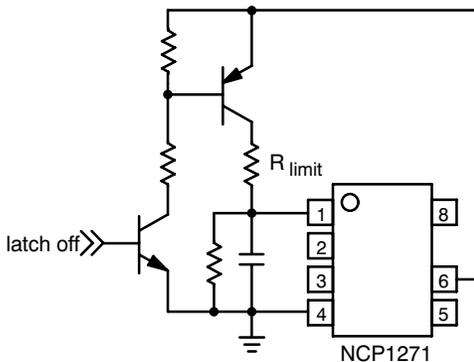


Figure 8. Simple Latchoff Circuit by Bipolar Transistors

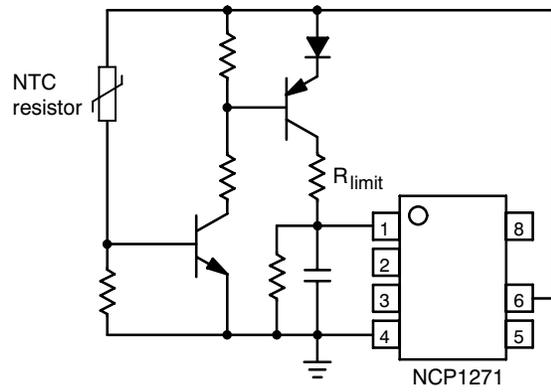


Figure 9. Overtemperature Protection Latch with a NTC Thermistor

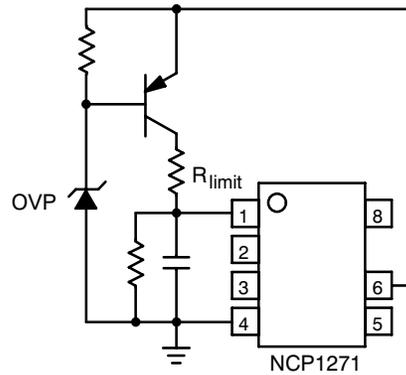


Figure 10. Output Overvoltage Protection Using the Auxiliary Winding

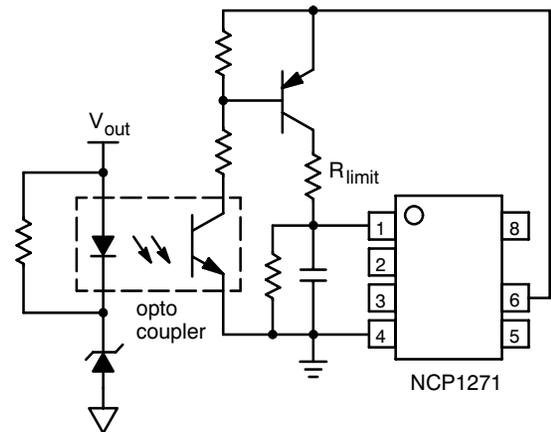


Figure 11. Output Overvoltage Protection Using an Optocoupler

It is important to note that when Pin 1 is open it sets the default skip level to 1.2 V. However, in this mode, pin 1 is internally pulled high to the Vskip-reset level (6.5 V typ). This only leaves about 1.5 V of noise margin before the part latches off. Therefore, if a skip level of 1.2 V is desired, then instead of leaving pin 1 open, it is always recommended to place a 28 kΩ resistor from pin 1 to GND. Then the skip level becomes 1.2 V ($28\text{ k}\Omega \times 43\text{ }\mu\text{A} = 1.2\text{ V}$), and the pin 1 voltage is also 1.2 V. This gives much better noise immunity and reduces the chance of falsely triggering the latch due to noise or leakage current from the external latch circuitry. Additionally, a small capacitor should be added to pin 1 to further increase the noise immunity.

HV Pin Protection Circuit

When the main power is interrupted in the application, the high voltage DC bus may potentially go negative in a short transient period. Since this is directly connected to pin 8, it could create a reverse current out of the HV Pin and could potentially damage the device. There are two easy solutions to this problem. The first is demonstrated in Figure 12. The inserted diode turns on when the HV Pin voltage goes below the VCC biasing voltage. This eliminates the chance of negative voltage on the HV pin. A second method is shown in Figure 13. Here, the inserted resistor limits the negative current to a low level and protects the HV pin. Either option works well, but for this demo board, a diode between VCC and HV was used.

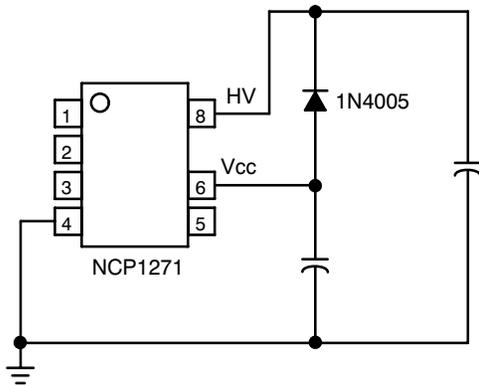


Figure 12. Protection Diode for HV Pin

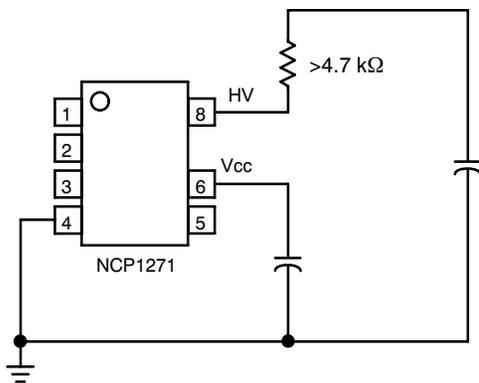


Figure 13. Protection Resistor on HV Pin

Layout Consideration

Figures 9-10 show the layout of the design. It is a single-layer PCB. As with any power converter, some care must be exercised with the design and layout. The following are some important guidelines.

1. Minimize the high-current loop and locate the IC controller outside the high-current loop to prevent malfunctioning of the IC internal logic due to strong magnetic fields from the high current.
2. Locate the decoupling capacitors close to the device to improve noise immunity.
3. Locate the VCC capacitor very close to the device to prevent the circuit from entering a UVLO fault condition because of noise.
4. Locate the output voltage sense resistor close to the output load points.
5. Minimize the current sense trace. It can become easily polluted with noise.
6. Minimize the distance between the feedback opto-coupler and controller because this trace is also easily polluted.
7. Minimize the distance between the MOSFET and controller because the PCB trace is high frequency and high current so it can easily pollute other parts of the circuit.

Additionally, there are three pins in the NCP1271 that may need external decoupling capacitors.

1. Skip/latch pin (Pin 1) – If the voltage on this pin is above 8.0 V, the circuit enters latch-off protection mode. Hence, a decoupling capacitor on this pin is essential to improve noise immunity. Additionally, a resistor should always be placed from this pin to GND to prevent noise from causing the pin 1 level from exceeding the latch-off level.
2. Feedback pin (Pin 2) – A small capacitor may be necessary here for improved stability and noise immunity.
3. VCC pin (Pin 6) – The NCP1271 maintains normal operation when VCC is above VCC(off) (9.1 V typical). If VCC drops below VCC(off), then the circuit enters UVLO protection and restarts after a double hiccup. Therefore, if VCC inadvertently drops below VCC(off) due to switching noise, then the circuit will recognize it as a fault condition. Hence, it is important to locate the VCC capacitor and a ceramic decoupling capacitor as close as possible to the NCP1271.

Measurements

Standby Performance

Thanks to the features in the NCP1271, the demo board power supply offers excellent no load and light load standby performance. The 230 Vac power consumption of the 57 W circuit is only 83 mW. And the input power at 230 Vac with 500 mW load is only 710 mW. Figure 14 shows the efficiency with output loads from 500 mW to 60 W at 120 Vac and 230 Vac.

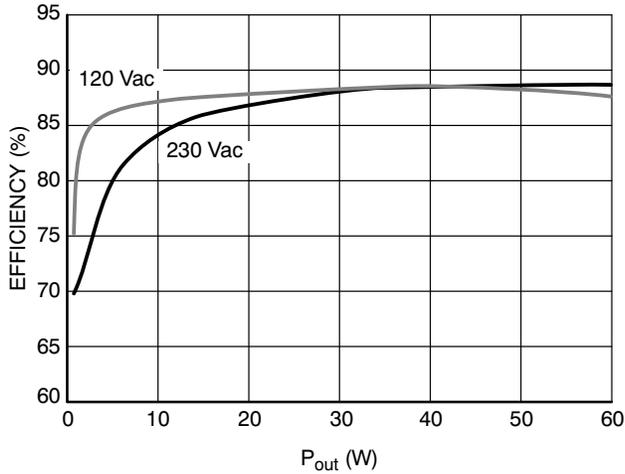


Figure 14. Efficiency of the NCP1271 Demo Board at Nominal Line Voltages

Dynamic Study

Figure 15 shows the startup transient waveforms of the circuit when the input is 110 Vac. A 4 ms soft-start is observed in the drain current. The V_{FB} drops below 3.0 V after 32 ms. Since this is shorter than the 130 ms fault validation time, the circuit does not enter fault condition and starts up normally.

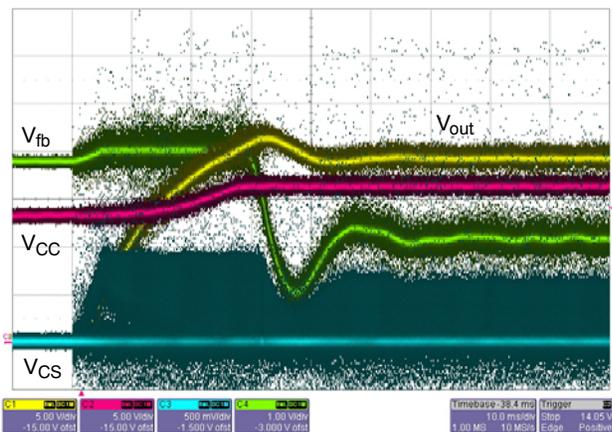


Figure 15. Startup Transient

Figure 16 shows the go-to-standby transition from full load operation. The output voltage (yellow trace) does not consume current and remains at 19 V, but the V_{CC} voltage drops from 16 V to 15 V because the V_{CC} auxiliary winding is not supplying current to the controller. The minimum V_{CC} voltage in the transition can be as low as 12 V. This is why the 16 V biasing voltage was selected to maintain V_{CC} above $V_{CC(off)}$ and prevent a V_{CC} reset.

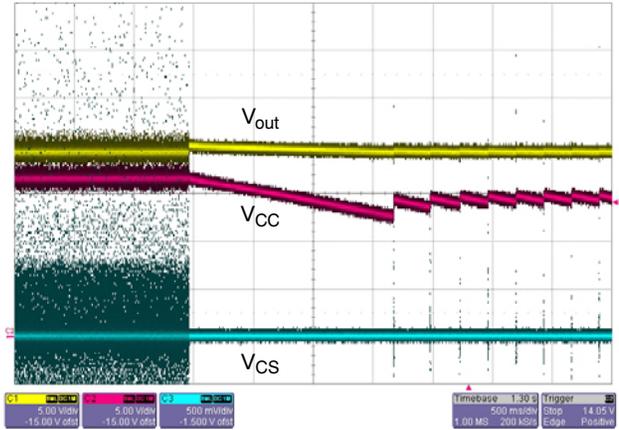


Figure 16. Operating to Standby

Short Circuit Protection Measurements

Figure 17 details the operation of the short circuit protection. The load steps from 60 W to 100 W, causing the peak current to increase to its maximum (1 V) as shown by the blue CS voltage. After approximately 130 ms, the controller shuts the power supply down and enters double hiccup fault operation (Figure 18). This provides very low power dissipation and protects the power components. When the short circuit fault is removed, the application recovers by executing a soft start and bringing the output back to 19 V.

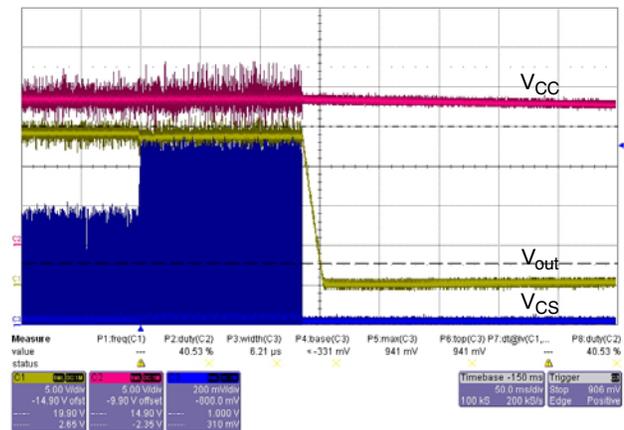


Figure 17. Short Circuit Protection is Activated When the Output Load Increases to about 100 W

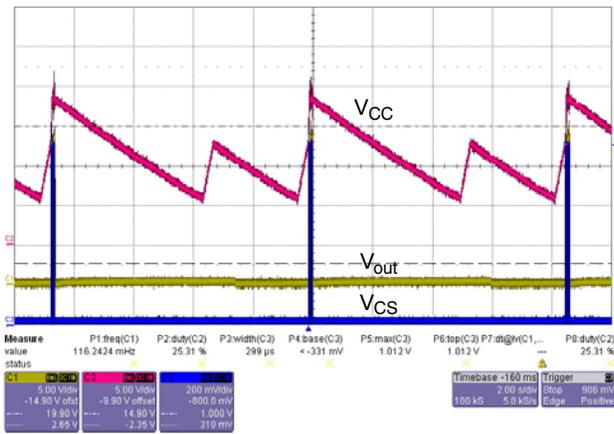


Figure 18. The Controller Enters Double Hiccup Fault Operation during a Continuous Short Circuit Event

Conclusion

A 57 W flyback power supply featuring over voltage and short circuit protection using the NCP1271 was demonstrated to have excellent light load power dissipation and active mode efficiency. The NCP1271's proprietary Soft-Skip™ operation offers low-audible-noise and excellent standby performance. The NCP1271 design worksheet, as well as other design aid resources, are available at www.onsemi.com.

AND8242/D

Appendix I: Bill of Materials for the NCP1271 19 V/3.0 A Example Circuit

| Designator | Qty | Part Number | Description | Manufacturer |
|----------------------------|-----|---------------------------------------------------|-------------------------------------------------------------------|--------------------|
| T1 | 1 | E3506-A | 3.0 A 508 μ H Common-Mode Filter | Coilcraft |
| T2 | 1 | CTX22-17179 | Custom Transformer 180 μ H 30:6:5, 2.5 μ H Max Leakage | Cooper/Coiltronics |
| IC1 | 1 | NCP1271D65R2 | 65 kHz Flyback PWM Controller, SO-7 | ON Semiconductor |
| IC2 | 1 | TL431AID | 2.5 V 1% Voltage Reference, SO-8 | ON Semiconductor |
| IC3-IC4 | 2 | SFH615AA-X007 | Optocoupler | Vishay |
| D1-D4 | 4 | 1N5406 | 3.0 A 600 V Diode, Axial 267-05 | ON Semiconductor |
| D5 | 1 | MMSZ914 | 1.0 A 100 V Diode, SOD-123 | ON Semiconductor |
| D6 | 1 | MRA4005T3 | 1.0 A 600 V Diode, SMA | ON Semiconductor |
| D7 | 1 | MURS160 | 1.0 A 600 V Diode, SMB | ON Semiconductor |
| D8 | 1 | MBR3100 | 3.0 A 100 V Schottky Diode, Axial 267-05 | ON Semiconductor |
| D10 | 1 | MZP4746A | 18 V @ 14 mA Zener Diode | ON Semiconductor |
| Q1 | 1 | SPP06N80C3 | 6.0 A 800 V N-MOSFET, TO-220AB | Infineon |
| R1 | 1 | P100KW-2BK | 100 k Ω 2.0 W, Axial 5% | - |
| R2 | 1 | CFR-25JB-10R | 10 Ω , 1/4 W Axial | Yageo |
| R5 | 1 | CRCW12063012F | 30.1 k Ω , 1206 | Vishay |
| R6 | 1 | CRCW120610R0F | 10 Ω , 1206 | Vishay |
| R7 | 1 | CRCW12065110F | 511 Ω 1206 | Vishay |
| R8 | 1 | WSL2512R2500FEA | 0.25 Ω 1.0 W 1% | Vishay |
| R9, R10 | 1 | CRCW12061691F | 1.69 k Ω , 1206 | Vishay |
| R11 | 1 | CRCW12061582F | 15.8 k Ω , 1206 | Vishay |
| R12 | 1 | CRCW12062371F | 2.37 k Ω , 1206 | Vishay |
| C1-C2 | 2 | PHE840MA6100MA04 | 0.1 μ F X2 Cap 10 mm Pitch | Evox Rifa |
| C3 | 1 | ECOS2GP820BA, EETED2G820BA, or EETXB2G820BA | 82 μ F 400 V Electrolytic | Panasonic |
| C4, C13 | 2 | ECA1EM101 | 100 μ F 25 V Electrolytic | Panasonic |
| C5 | 1 | 630MMB103J | 10 nF 630 V Film Cap | Rubycon |
| C6-C7 | 1 | VJ1206Y122KXXA | 1.2 nF 25 V, 1206 | Vishay |
| C9-C10 | 3 | 025YXG220M12.5X30 | 2200 μ F 25 V Electrolytic | Rubycon |
| C11 | 1 | ERO610RJ4100M | 1.0 nF 1.0 kV 5.0 mm Pitch Y2 Cap | Evox Rifa |
| C12 | 1 | VJ1206Y154KXXA | 0.15 μ F 25 V Ceramic | Vishay |
| Fuse | 1 | 1025TD2-R | 250 V 2.0 A Tie Delay Fuse | Cooper Fuse |
| Heatsink | 1 | 590302B03600 | Heatsink for TO-220 Package | Aavid |
| Heatsink Insulation | 1 | 4672 | TO-220 Mica Insulation | Keystone |
| AC Connector | 1 | 770W-X2/10 | IEC60320 C8 Connector | Qualtek |
| DC Connector | 1 | 26- 60- 4030 or 009652038 | 3-Terminal 3.96 mm Pitch Male Header | Molex |
| Standoff | 4 | 4804 K | Standoff M/F Hex 4-40 Nyl 0.750" | - |
| Heatsink Mechanic | 1 | 30F698 | 4-40 1/4 Inch Screw | - |
| Heatsink/Standoff Mechanic | 5 | 31F2106 | 4-40 Screw Nuts | - |
| Nylon Washer | 1 | 3049 | Nylon Shoulder Washer #4 | - |

AND8242/D

Appendix II: NCP1271 57 W Adaptor Layout

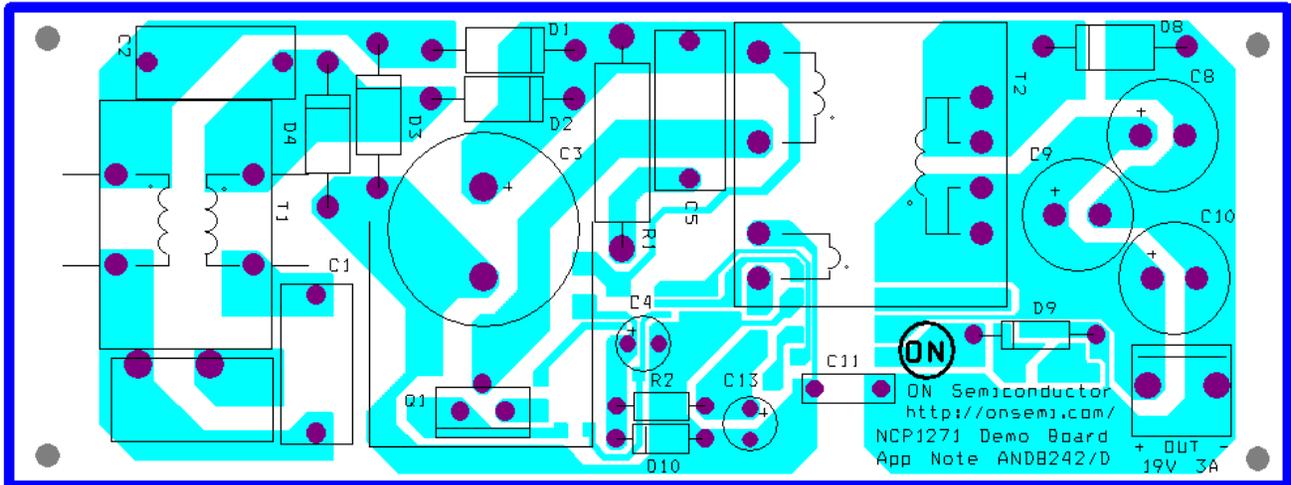


Figure 19. Top View

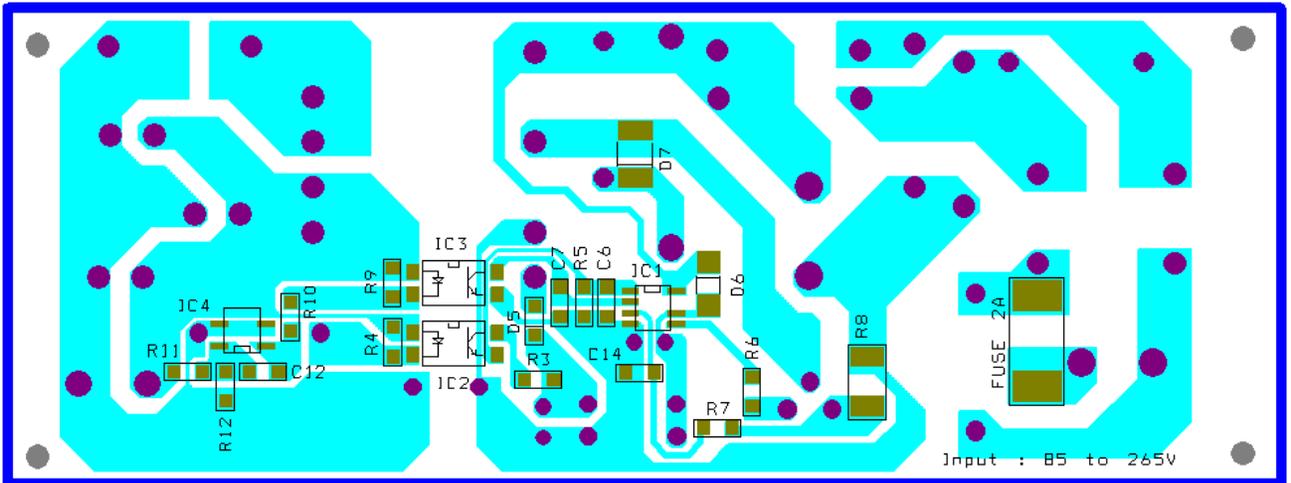


Figure 20. Bottom View

Soft-Skip is a trademark of Semiconductor Components Industries, LLC (SCILLC).

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:
Literature Distribution Center for ON Semiconductor
P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5773-3850

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>

For additional information, please contact your local Sales Representative