



Is Now Part of



ON Semiconductor®

**To learn more about ON Semiconductor, please visit our website at
www.onsemi.com**

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

AN-8020

Integrated Slew Rate Controlled Switch Optimizing 1V Core in Mobile Systems

FPF1018, IntelliMAX™, a slew-rate-controlled load switch, guarantees that mobile systems operate with more reliable and stable power at very low voltage core line for steady and transient operations than current existing discrete solutions.

Mobile System Power Trend and Requirements

Recent mobile systems require the very low voltage core, realized by smaller process geometries, to employ more function blocks with low power consumption and improve performance of micro-processors. For the mobile systems to perform properly, low voltage power must be delivered efficiently and stably, even with high currents, whether it's transient or steady state. As needed core voltage decreased, it became important to conform to stringent regulations and transient specifications. In fact, V_{CORE} of MAPs (multimedia application processors) in mobile applications is becoming lower and MAPs with V_{CORE} of 1V have appeared, which requires stable power within range of 0.9V ~ 1.1V at least. Figure 1 describes an example power block of MAP that has 1V cores. 1V is converted by buck converter from battery and delivered to V_{CC1} for Function Block 1 and the other 1V line goes to V_{CC2} passing through load switch. In this kind of mobile application, load switch for V_{CORE} as low as 1V in mobile system must satisfy a few conditions to deliver low voltage power efficiently and follow the strict regulation for stable operation of chipsets.

First, R_{ON} (on state resistance) of the switch should be low enough to give enough head room to V_{CORE} , which could have 1V with $\pm 3\%$ or $\pm 5\%$ variance due to the characteristics of buck converter, to ensure that it never causes abnormal operation of the function block. Second, a reliable load switch prevents inrush currents to drop the input voltage whose line is connected to the other V_{CORE} line to drop below 0.9V and to cause malfunction of the other function block during startup operation. Last, when switch turns off, the discharge path of the load switch helps to discharge the remaining voltage at the output capacitors to enable reliable power off and keep the chipset from abnormal operations.

Although these solutions; such as low R_{ON} , inrush current control, and discharge function, can be embodied in discrete components; an integrated load switch is recommended in mobile applications. This application note examines and explains the methods to maintain stable power of the chipset; compares and analyzes FPF1018, an integrated load switch with a V_{IN} range of 0.8~1.8V to optimize 1V core line, and discrete solutions; and explains why integrated, very low voltage rated, slew rate controlled, load switch is necessary in mobile applications.

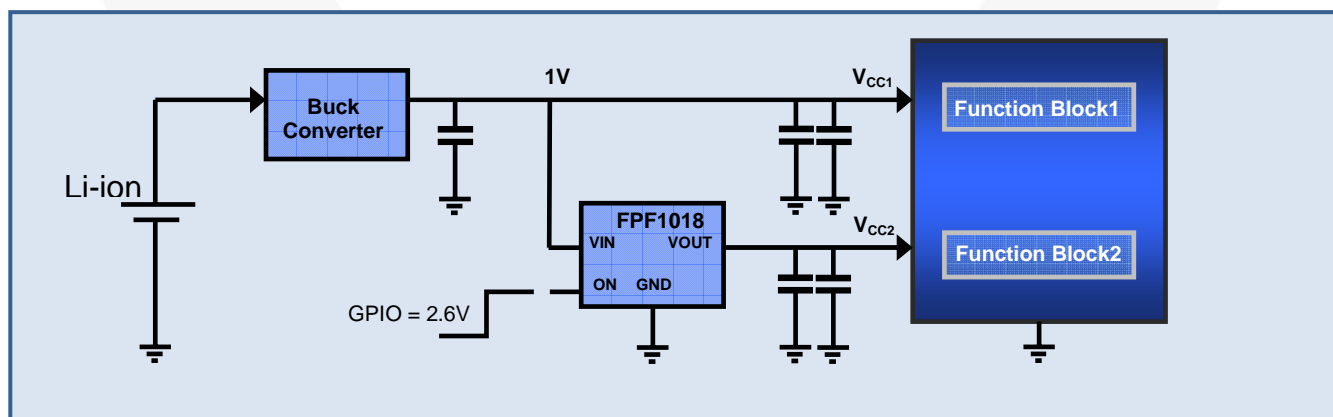


Figure 1. 1V Power to V_{CORE} of Chipset in Mobile Systems

Low Power Consumption and Stable Steady-State Operation

One of the most important things that determine efficient power is R_{ON} , which causes voltage drop across the switch and affects V_{CORE} of the chipset directly and power consumption of switch during operations. For this reason, mobile systems mostly use N-ch devices with low R_{ON} for discrete solutions or integrated load switches, such as FPF1018, since $R_{DS(on)}$ of P-ch devices is higher compared to N-ch FET with the same die size and provides less head room for V_{CORE} line and higher power consumption. This section compares R_{ON} , voltage drop, and power consumption across the integrated load switch, FPF1018, and an N-ch FET and explains why securing enough head room is important. In the case of MAP applications, a regulator produces 1V power that varies between 0.95V and 1.05V from battery and the chipset's allowable core voltage has a tolerance of $\pm 10\%$, which means it has 0.05V head room for the worst case. The voltage across the load switch decreases the head room for stable operation of MAP.

Table 1. V_{out} and P_d Comparison

	V_{IN} (V)	V_{OUT} (V)	I_{LOAD} (A)	R_{ON} (m Ω)	P_D (mW)
N-ch FET	1.00	0.97	0.30	96.70	8.70
FPF1018	1.000	0.987	0.300	40.000	3.600

Figure 2 and Figure 3 depict an integrated load switch and discrete solution. As shown in Table 1, the measured R_{ON} of FPF1018 and N-ch FET in a SC-70 package with similar dimensions to the FPF1018 in a 2X2 MLP package are 40m Ω and 96.7m Ω , respectively, when input voltage is 1V, GPIO voltage is 2.6V, and load current is 300mA for both cases. In the case of FET, if V_{GS} of 2.6V is applied and 1V is applied to V_{IN} pin, the voltage across the FET is 30mV and power consumption is 8.7mW. The 30mV voltage drop gives only 21mV margin to operate stably when V_{IN} is 0.95 from buck converter in the worst case. Whereas, in the case of FPF1018, when V_{IN} of 0.95V (the worst case) is applied and V_{ON} is 2.6V, there's only 12mV voltage drop and power consumption of 3.6mW across the switch, which are very low values compared to discrete solution. This gives

38mV head room for the margin. Even though buck converter is under unstable conditions, FPF1018 guarantees reliable operation during steady-state operations with low R_{ON} . So with a very low voltage operating load switch, FPF1018 guarantees more reliable on-state operation and less power consumption of load switch and gives more head room for V_{CORE} margin delivered to processors.

Stable Operation During Startup

The basic purpose of using load switches in mobile system is to save power and lengthen battery life by shutting off the switch when the function block is not being used. As shown in Figure 6, Function Block2 can be turned on/off by the usage needs. Due to this fundamental characteristic of the load switch, the systems would be in startup often when system needs to enable function block, which means this turn-on characteristic is one of the important factors that can affect system operation. In fact, if rising time of V_{CORE} is fast and has big capacitive load, a surge current (inrush current) would occur into the output capacitors, which stabilize the V_{CORE} and chipset operation during steady-state operation. While this inrush current charges the output capacitors up, it causes input voltage to drop below the minimum voltage range of 0.9V, which guarantees stable operation of chipset. This condition may turn off or reset the other functional blocks connected to the same 1V line, which is the situation described in Figure 6. For the system to turn Function Block2 in Figure 6 on stably and not to cause abnormal behaviors of Function Block1 while it is working, rise time could be adjusted.

$$I_{total} = I_C + I_{LOAD} = C_{OUT} \frac{dV_{out}}{dt} + \frac{V_{out}}{Z_{LOAD}} \quad (1)$$

C_{OUT} should be large enough for stable steady-state operation and cannot be smaller than that set by the system, but the rise time of V_{CORE} can be adjusted. According to Equation 1, long enough rising time guarantees the system can reduce inrush current and make input voltage droop negligible. In discrete solutions, rise time could be lengthened by adding a resistor and capacitor on the gate pin, such as shown in Figure 3. Adding resistor and capacitor makes FET turn on slowly.

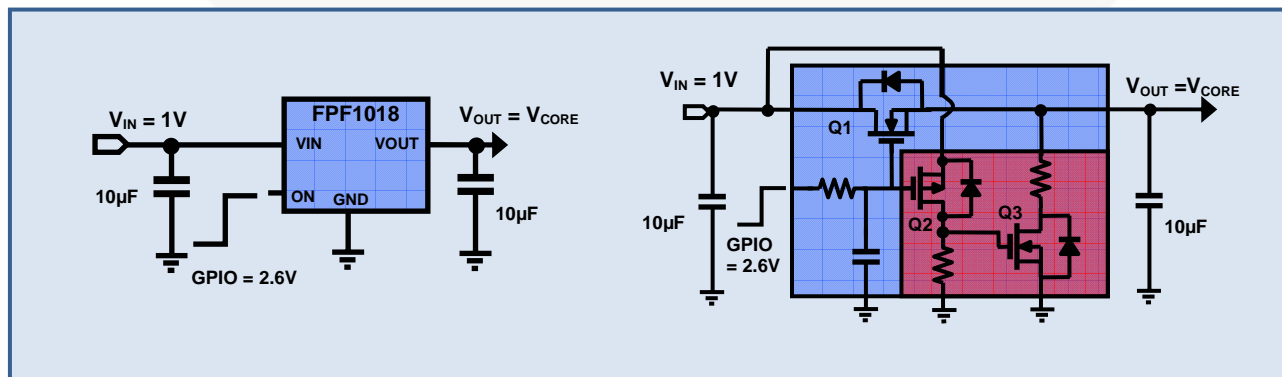


Figure 2. Integrated Load Switch

Figure 3. Discrete Solution

To compare V_{IN} drops in two situations; short rise time and long rise time, note Figure 4 and Figure 5. Figure 4 shows that without additional RC components, V_{IN} drop is 440mV, which can cause problems with Function Block1 in Figure 6. It needs one resistor and one capacitor more, which occupy PCB (printed circuit board) space, at the gate pin to lengthen the V_{OUT} rising time, reduce inrush current, and minimize the V_{IN} drop; but it needs trial and error to find the appropriate RC values for the application.

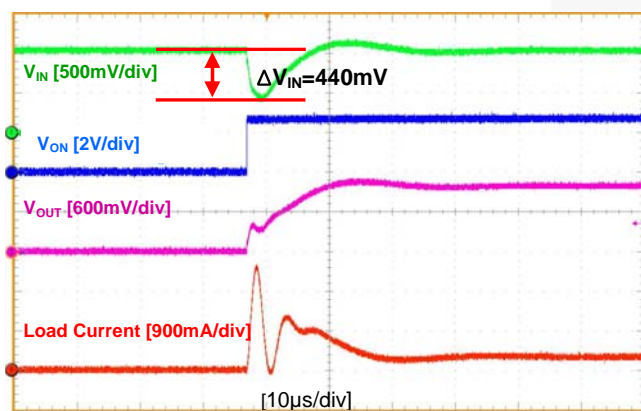


Figure 4. Turn-On: N-ch FET without RC at Gate

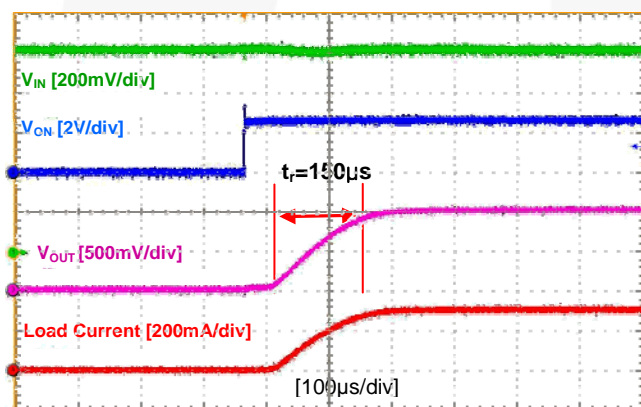


Figure 5. Turn-On: FPF1018

On the other hand, FPF1018, a monolithic slew-rate-controlled switch, has built-in long slew rate of 150μs, which minimizes V_{IN} droop. As seen Figure 5, it has long enough rise time to minimize V_{IN} drop and guarantee stable normal operation of Function Block 1 in Figure 6 during startup. The long slew rate of FPF1018 offers more reliable startup operation without additional passive components over discrete solutions with less PCB space.

Reliable Power Off

Power switches are used for powering for operation, and isolation for power saving. The discharge path of a load switch makes sure there are no charges stored and voltage remaining at output capacitors that can cause abnormal operations of chipsets after turn-off. When Function Block2 in Figure 6 and the switch are turned off, the load condition is under no-load condition and load capacitors would discharge naturally. But natural discharging takes a very long time, as shown in Figure 7, if the load capacitors are big enough. If V_{CORE} is still alive, the system may register the function block as still in on state and command it to operate. This creates a malfunction in this situation because function block is not powered. To avoid this abnormal operation after switch turning-off, V_{CORE} must be pulled down to ground immediately.

Figure 7 shows the remaining voltage of discrete solution due to a large output capacitor at V_{OUT} after turn-off and Figure 8 shows V_{OUT} decreasing down to 0V fast during turn-off. For discrete solutions, discharge function could be realized by placing appropriate FETs and resistors at the output of load switch, but this discharge function by discrete components takes larger area on the PCB than the one implemented in a monolithic load switch. A discrete solution is described in the red box, in Figure 3, and needs two more resistors, one more P-ch FET, and one more N-ch FET, while monolithic load switches don't need any extra components on PCBs. Figure 9 and Figure 10 show the space difference between the load switches composed of discrete components and a monolithic load switch and additional components on PCB for each solution.

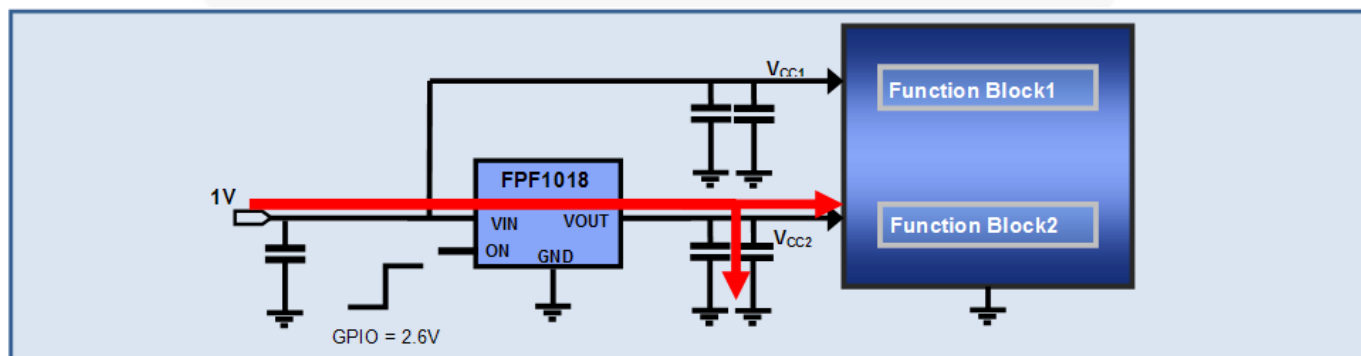


Figure 6. Current Flowing Path During Turn-On

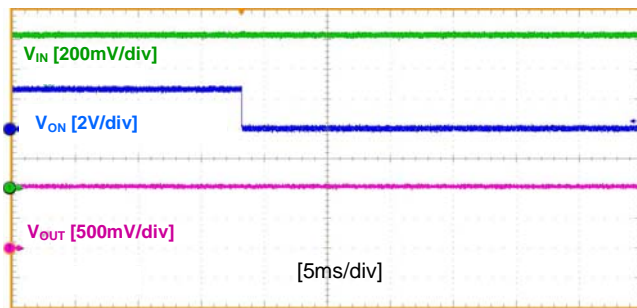


Figure 7. Turn-Off: N-ch FET without Discharge Function at No Load

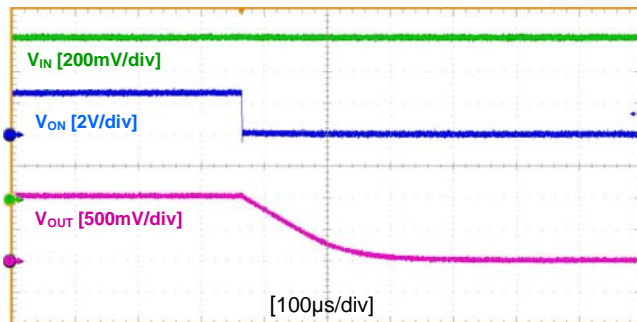


Figure 8. Turn-Off: FPF1018 at No Load

Constituting a discharge path at 1V power supply line with discrete components, note that the discrete discharge path would not be perfect due to $V_{GS(th)}$ of N-ch MOSFET, Q3 in Figure 3. Typical $V_{GS(th)}$ of N-ch FET is 0.7V, but $V_{GS(th)}$ ranges from 0.4 (minimum) to 1.5V (maximum) with normal distribution. Although most products used for mobile system have a $V_{GS(th)}$ less than 1V, it is possible that $V_{GS(th)}$ of some MOSFETs resides above 1V, which may not allow to activate discharge path. So the discharge path with discrete solution is not perfect with N-ch FET with $V_{GS(th)}$ of 1.5V maximum. Unfortunately there's no FET with maximum $V_{GS(th)}$ less than 1V in current semiconductor industry. So the discharge path for 1V core is not perfect with discrete components. However, FPF1018, an integrated load switch, ensures reliable discharge with internal 60Ω pull-down resistor and takes a very small PCB space, which is crucial for mobile applications.



Figure 9. FPF1018 Evaluation Board

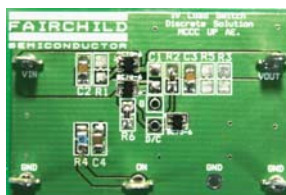


Figure 10. Discrete Solution Evaluation Board

Conclusion

This application note covered features and functions of the lowest V_{IN} rated load switch in current industry, FPF1018, over discrete solutions in mobile system and necessities of them. To conform to the strict regulations and transient operation specifications, it would be necessary for load switch to have low R_{ON} , long enough slew rate, and perfectly guaranteed discharge path. These features and functions give FPF1018 decided advantages over discrete solutions at 1V core in mobile systems.

Author

Harry HeeYeol Jeong, Fairchild Semiconductor

Related Datasheets

FPF1015/6/7/8 — IntelliMAX™ 1V Rated Advanced Load Management Products

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION.

As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada

Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910

Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com

Order Literature: <http://www.onsemi.com/orderlit>

For additional information, please contact your local
Sales Representative