



Universal Input, 50W, 5 Output PSU

Device	Application	Input Voltage	Output Power	Topology	I/O Isolation
NCP1308, LM2575	Medical Equipment	85 to 265 Vac	40 W average, 50 W peak	Quasi-Resonant Mode Flyback	Yes – 3kV

Other Specifications

	Output 1	Output 2	Output 3	Output 4
Output Voltage	12 VDC	-12 VDC	5 VDC	3.3 VDC
Ripple	+/- 20mV	+/- 20mV	2% - 5%	2% - 5%
Nominal Current	2.5 A	150 mA	900 mA	150 mA
Max Current	3 A	300 mA	1.2 A	300 mA
Min Current	10 mA	10 mA	10 mA	10 mA

PFC (Yes/No)	No
Minimum Efficiency	75 % at nominal load
Inrush Limiting / Fuse	Yes - both
Operating Temp. Range	0 to +60°C
Cooling Method/Supply Orientation	Convection

Others	5 th Output with 350 Vdc @ +/- 20 V at 50 mA max.
--------	--

Circuit Description

This Design Note features a universal AC input, 50 watt peak output flyback power supply with 5 separate output voltages. The 3.3 volt and 5 volt outputs are derived from the +12 volt output using identical LM2575 monolithic buck regulators. The 350 volt output is derived from a “slave” secondary flyback winding on the main transformer. ON Semiconductor’s NCP1308 controller provides for quasi-resonant Mosfet switching and current mode control of the flyback topology for high conversion efficiency and low noise generation. Voltage sensing and regulation for the main +12 volt output is achieved utilizing the conventional TL431A error amp and optocoupler feedback scheme. The negative 12 volt output achieves satisfactory regulation via a tightly coupled secondary winding with the main +12 V output’s secondary winding (bifilar wound). The 3.3 V and 5 V outputs require minimal components utilizing the LM2575 buck regulators and off-the-shelf ferrite inductors.

Key Features

- Over-current, over-voltage, and over-temperature protection.
- Input common and differential mode EMI filter for agency EMI compliance.
- NTC thermistor for inrush current limiting at initial supply turn-on.
- Pi-network ripple filters (L2, L3) on the +/-12 V outputs for low output noise and ripple.
- Main flyback transformer designed with common industry standard ETD29 ferrite core.



MAGNETICS DESIGN DATA SHEET

Project : 50W, 5 output power supply

Part Description: Quasi-resonant flyback transformer, 50W, +/-12Vout/350Vout

Schematic ID: T1

Core Type: ETD29 (Ferroxcube 3C95 material or equivalent)

Core Gap: Gap for 400 uH +/- 5% across pins 13 to 1


Inductance: 380 to 420 uH nominal across primary (pins 13 to 1)

Bobbin Type: ETD 13 pin horizontal pc mount (Ferroxcube PC1-29H)

Windings (in order):


Winding # / type/pins	Turns / Material / Gauge / Insulation Data
Aux winding (12 - 2)	5 turns of # 26HN spiral wound evenly over bobbin. Self-leads to pins. Insulate for 1 kV to next winding.
Primary (13 - 1)	42 turns of #26HN over one full bobbin layer; Self-leads to pins; insulate for 3 kV to next layer.
+/-12V secondary (9,8, - 4,5)	5 turns of 5 strands #25HN; one strand should be green for -12V winding; flat-wind over 1 layer with 3.5 mm approximate end margins. Winding ends should be cuffed with tape. Self-leads to pins with 4 wires per pin on +12 strands. Insulate with tape for 3 kV to next winding.
350V secondary (7 - 6)	135 turns of #38HN over 1 layer; self-leads to pins. Final tape insulation to 3kV.

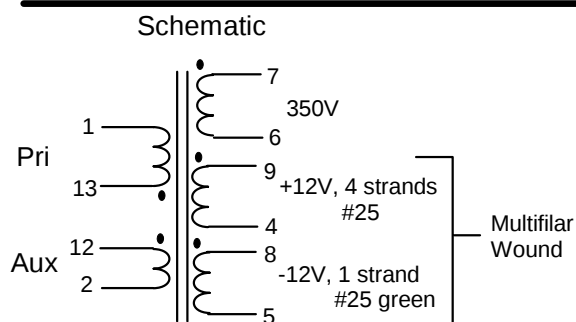Hipot: 3 kV primary/aux to all secondaries. Vacuum varnish.



Lead Breakout / Pinout

Bottom (pin side) view

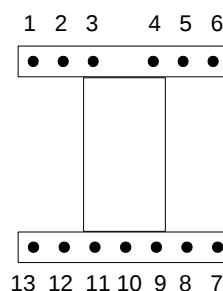

© 2007 ON Semiconductor.

Disclaimer: ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

Design note created by Frank Cathell, e-mail: f.cathell@onsemi.com